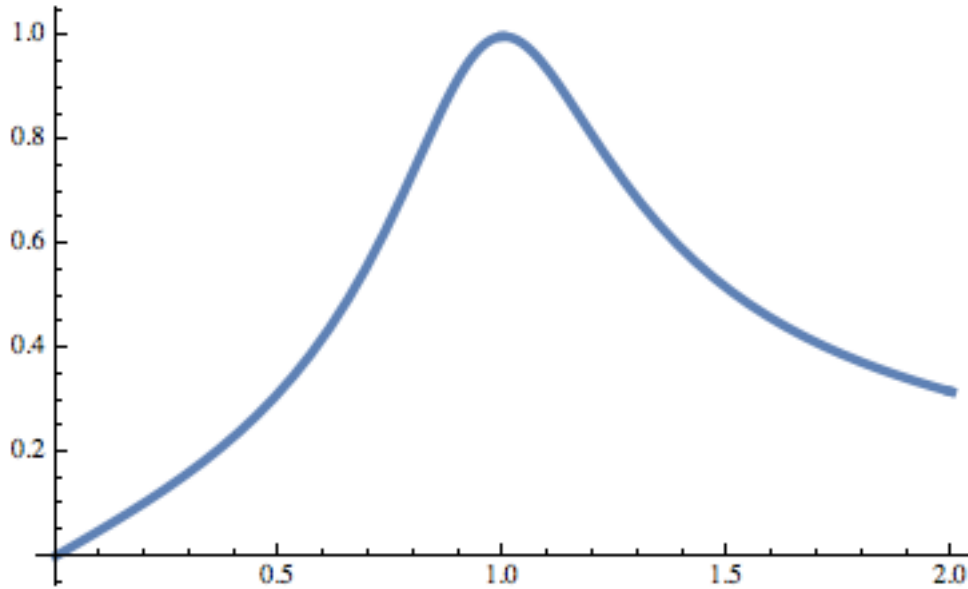



Bode Plots for RLC Series Circuits (linear scale)

$|H(\omega)|$



ω/ω_r


θ
(deg)

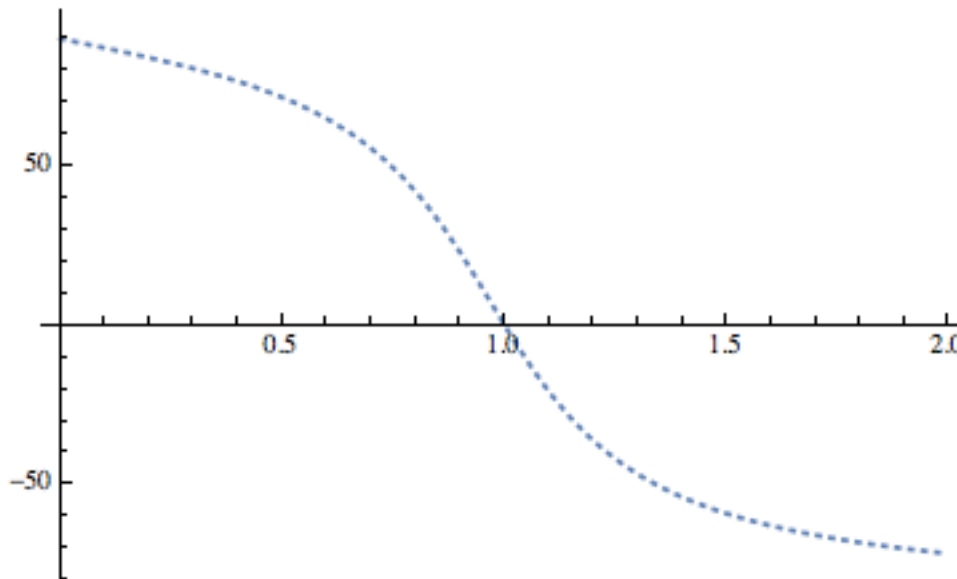

ω/ω_r

Bode Plots for RLC Series Circuits (log)

$|H(\omega)|$

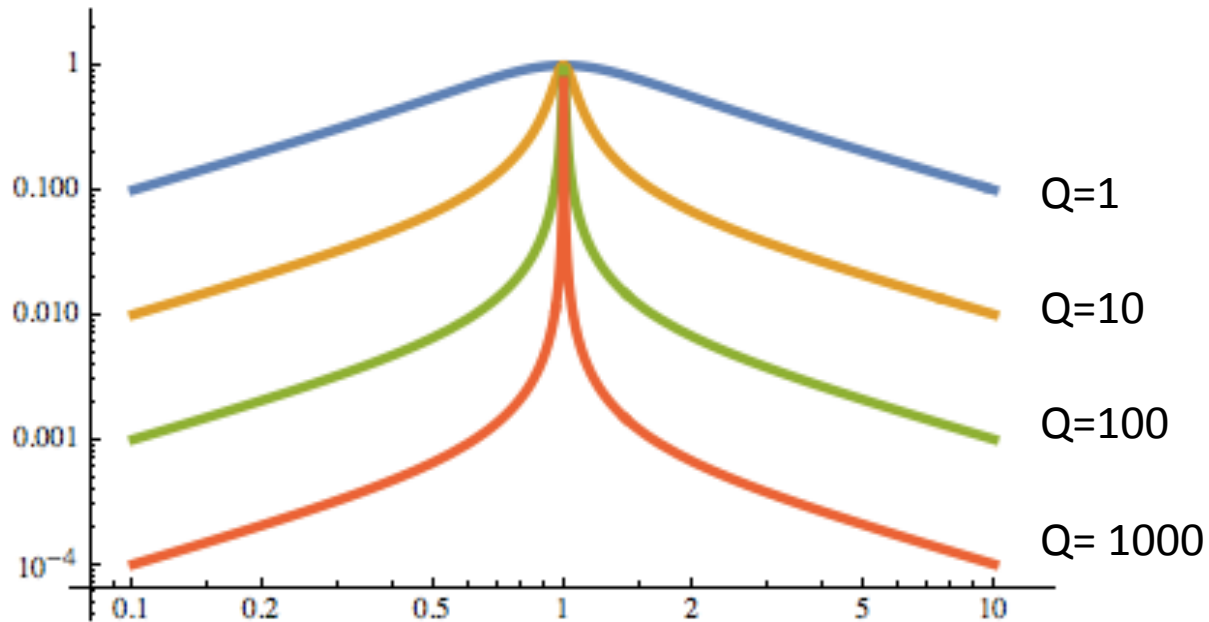

θ
(rad)

