
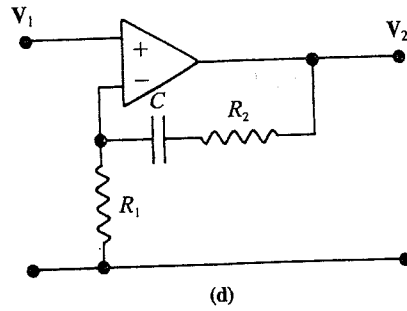


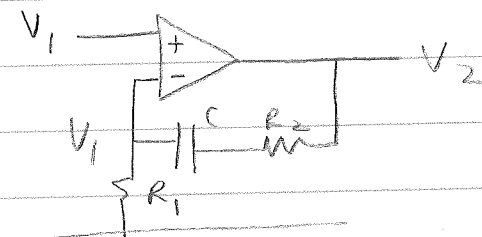

Find $G(j\omega)$, corner frequency
 Sketch Bode plot

Ideal op-Amp Rules (ω / feedback) : $V_+ = V_-$
 $I_+ = I_- = 0$

8.6) a) Find $G(j\omega)$ for



Sketch $|G|$


Find corner frequency

$$V_1 = \frac{R_1}{R_1 + R_2 + j\omega C} V_2$$

$$G(j\omega) = \frac{V_2}{V_1} = \frac{R_1 + R_2 + 1/j\omega C}{R_1} = \frac{1 + (R_1 + R_2)j\omega C}{j\omega R_1 C}$$

For ω small $G_L \sim 1/j\omega R_1 C$

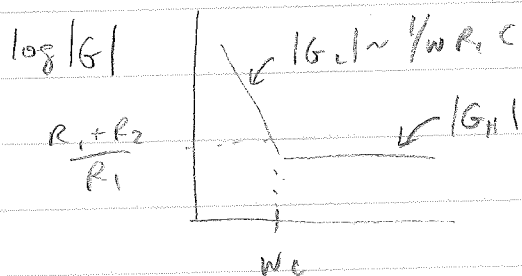For ω large $G_H \sim \frac{R_1 + R_2}{R_1}$




ω_c


corner for $\frac{R_1 + R_2}{R_1} = \frac{1}{\omega_c R_1 C}$

$$\omega_c = \frac{1}{(R_1 + R_2)C}$$

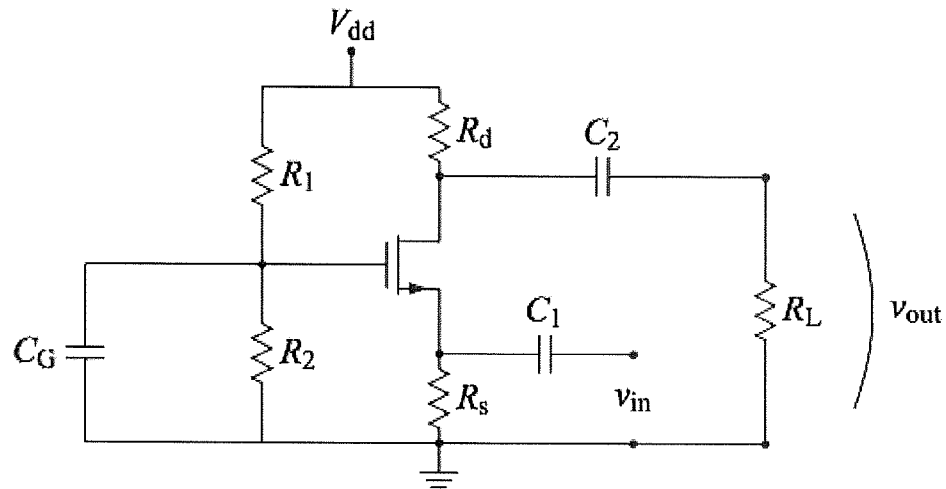Derive the expressions for the voltage gain a , the current gain g , the input impedance Z_{in} , and the output impedance Z_{out} for the common-gate amplifier.




Common gate amplifier


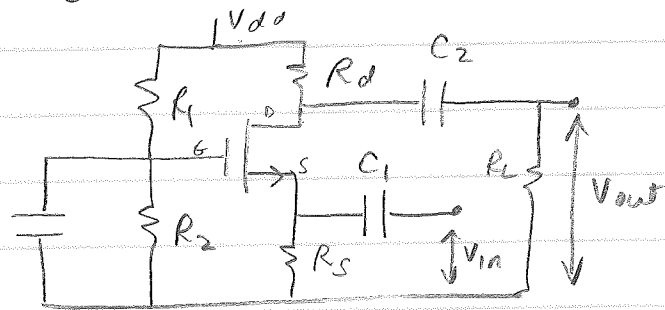


How to

Short caps

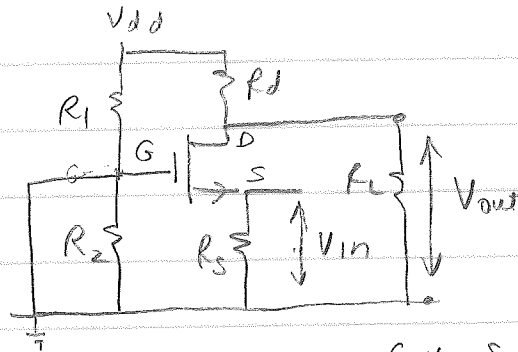


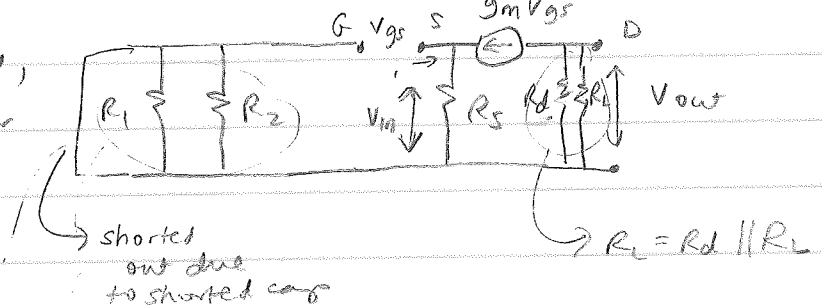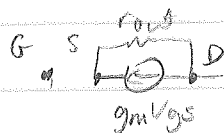Short supply to gnd,
insert transistor model



$$V_{in} = -V_{gs}$$

$$V_{out} =$$

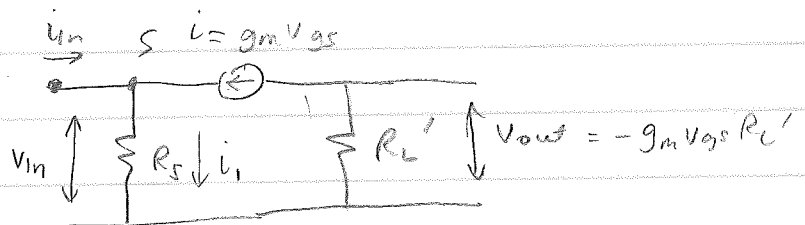

$$A = \frac{V_{out}}{V_{in}} = \frac{-g_m V_{gs} R_L'}{-V_{gs}} = g_m R_L'$$

$$I_1 = \frac{V_{in}}{R_S} = \frac{-V_{gs}}{R_S}$$

$$= g_m V_{gs} + I_{in}$$

$$\Rightarrow I_{in} = -\frac{V_{gs}}{R_S} - g_m V_{gs}$$

$$g = \frac{I_{out}}{I_{in}} = \frac{V_{out}/R_L}{-\frac{V_{gs}}{R_S} - g_m V_{gs}}$$

$$= \frac{-g_m V_{gs} R_L'/R_L}{-\frac{V_{gs}}{R_S} - g_m V_{gs}} = \frac{g_m R_L'/R_L}{g_m + 1/R_S}$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{-V_{gs}}{-V_{gs}(g_m + 1/R_S)} = \frac{R_S}{1 + g_m R_S}$$

$$(R_L \rightarrow \infty) \\ Z_{out} = \frac{V_{out}}{I_{out}} = \frac{-g_m V_{gs} R_L}{-g_m V_{gs}} = R_L$$

The three-input OR gate follows the Boolean statement $Q=A+B+C$

- a. Write a truth table for this gate.
- b. Write the Boolean statement for $\overline{Q}$ and implement the result using 2-input NAND gates and inverters.

3-input OR

$$Q = A + B + C$$

Want in terms of NANDs

a)

A	B	C	Q
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

b) De Morgan

$$\begin{aligned}
 Q &= \overline{A + B + C} = \overline{A + B} \cdot \overline{C} \\
 &= (\overline{A} \cdot \overline{B}) \cdot \overline{C} \\
 &= \overline{\overline{\overline{A} \cdot \overline{B}}} \cdot \overline{C} \quad \rightarrow \text{NAND} \\
 &= \overline{\overline{\overline{A} \cdot \overline{B}} \cdot C} \quad \text{NAND}
 \end{aligned}$$

