

Duke University  
Department of Physics

Physics 271

Spring Term 2017

## WUN2K FOR LECTURE 1

These are notes summarizing the main concepts you need to understand and be able to apply.

### DC circuits

- Current describes movement of charge:  $I = \frac{dq}{dt}$ .
- Potential  $V$  is potential energy per charge (gravitational potential is a good analogy). We will assume that potential is the same anywhere inside a conductor. In particular, we'll assume it's the same everywhere in a wire.
- An “electromotive force (EMF)” (not strictly a force)  $\varepsilon$  is a charge pump that maintains a potential across a conductor. An ideal EMF or voltage source maintains a fixed potential. We approximate a battery, power supply *etc.* as an ideal voltage source in series with an internal resistance.
- Ohm's Law for linear resistors:  $V = IR$  (it is *not* a universal law). The resistance  $R$  depends on the properties of the object:  $R = \frac{\rho l}{A}$ , where  $\rho$  is resistivity (property of the material),  $l$  is the length, and  $A$  is the cross-sectional area.
- Power dissipated in a circuit (generally to heat) according to  $P = VI$ . For an Ohm's Law case,  $P = I^2 R$  through a resistor.
- Resistors in series can be treated as an equivalent resistance  $R_{\text{eq}} = \sum_i R_i$ . Two resistors  $R_1$  and  $R_2$  in parallel can be treated as an equivalent resistance  $R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$ .

**Remember that abstractions are leaky!** (but useful).