

## WUN2K FOR LECTURE 19

These are notes summarizing the main concepts you need to understand and be able to apply.

- *Operational amplifiers* are the standard implementation of a high-input-impedance, low-output-impedance, high open-loop gain amplifier introduced in lecture 10. They are usually employed with negative feedback. Their transfer functions are typically those of low-pass filters with gain. Standard notation is  $A(j\omega)$  for open-loop gain,  $H(j\omega)$  for closed-loop gain, and  $G(j\omega)$  for approximate closed-loop gain.
- The rules for ideal op-amps (with negative feedback) are:
  1. The current drawn by both inputs is zero.
  2. The op-amp does whatever it needs to do at the output to make the voltage difference between the inputs zero.

A real op-amp doesn't follow these rules perfectly, but the rules are very helpful for understanding circuit behavior.

- The ideal op-amp rules can be used to understand and devise many useful circuits. Some examples:
  - Noninverting amplifier: feedback network with  $R_2$  between output and  $V_-$  input,  $R_1$  between  $V_-$  input and ground. The gain is  $G(j\omega) = \frac{R_2+R_1}{R_1}$ .
  - Inverting amplifier: feedback network with  $R_1$  between input and  $V_-$  input,  $R_2$  between  $V_-$  input and output. The gain is  $G(j\omega) = -\frac{R_2}{R_1}$ .

- Current summing junction: with a resistor  $R$  between  $-$  input and output,  $V_{\text{out}} = -RI$ . One can sum current sources, or also sum voltages by putting them across resistors in parallel at the input.
- Differentiator: replacing  $R_1$  of the inverting amplifier with a capacitor results in a circuit with  $G(j\omega) = -j\omega RC$ , which is a high-pass filter that differentiates at low frequency. In combination with the open-loop low-pass properties of the op-amp, one gets an (active) band-pass filter.
- Integrator: replacing  $R_2$  of the inverting amplifier with a capacitor results in a circuit with  $G(j\omega) = -\frac{1}{j\omega RC}$ , which is a low-pass filter that integrates at high frequency. In combination with the open-loop low-pass properties of the op-amp, one gets a lower-gain (active) low-pass filter.