

WUN2K FOR LECTURE 3

These are notes summarizing the main concepts you need to understand and be able to apply.

- **Equivalent Circuits:** Thevenin's theorem states the behavior of any 2-terminal network containing voltage sources, current sources and resistors can be reproduced by an ideal voltage source supplying voltage V_{Th} in series with a *Thevenin equivalent resistance*, R_{Th} . The *Norton equivalent* circuit is an ideal current source supplying current I_N in parallel with a Norton equivalent resistance R_N . It can be shown that $R_N = R_{Th}$ for the same network.
- How to find Thevenin and Norton equivalents for a given network:
 - The Thevenin equivalent voltage is $V_{Th} = V_{AB}(\text{open})$, the open-circuit voltage across the terminals A and B.
 - The Norton equivalent current is $I_N = I_{AB}(\text{short})$, the short-circuit current across terminals A and B.
 - $R_{Th} = V_{Th}/I_N$. However, the faster, almost-always-more-convenient method of finding R_{Th} is to short all the EMFs in the network and open all the current sources, and just find the equivalent resistance.
- Measurement devices such as voltmeters and oscilloscopes can be treated as Thevenin equivalent devices with very large ($\sim 10^6 \Omega$ or greater) R_{Th} .
- Error propagation reminder: if you derive quantity $w = f(x, y, z, \dots)$ from measured quantities x, y, z, \dots known with uncertainties $\Delta x, \Delta y, \Delta z, \dots$ respectively, *assuming uncorrelated uncertainties*, the uncertainty on w is given by $\Delta w = ((\frac{\partial f}{\partial x})^2(\Delta x)^2 + (\frac{\partial f}{\partial y})^2(\Delta y)^2 + (\frac{\partial f}{\partial z})^2(\Delta z)^2 + \dots)^{1/2}$.