

## WUN2K FOR LECTURE 5

These are notes summarizing the main concepts you need to understand and be able to apply.

- For AC circuits, in which we have sinusoidally varying currents  $I(t)$  and voltages  $V(t)$ , it's very useful to treat them as complex numbers,  $\hat{c}(t) = c_0 e^{j(\omega t + \theta)} = c_0 e^{j\theta} e^{j\omega t}$ . The *physical* variables are real, and correspond to the real (or imaginary) parts of the complex quantities. A complex number can be considered to be a vector in the complex plane, with real component  $c_0 \cos(\omega t + \theta)$  and imaginary component  $c_0 \sin(\omega t + \theta)$ . Since angle of this vector with respect to the real axis is  $(\omega t + \theta)$ , we can think of this vector as sweeping around the complex plane counter-clockwise as  $t$  increases. This kind of vector is called a *phasor*. Its initial angle is  $\theta$ , it rotates with angular frequency  $\omega$ , and its magnitude is  $c_0$ . Phasors are very useful for combining signals by superposition, because they behave just like vectors.
- Another useful concept that applies to AC circuits is that of *complex impedance*  $\hat{Z}$ , which is a kind of generalized resistance used in an AC-analog of Ohm's Law for sinusoidally time-dependent circuits,  $\hat{V}(\omega) = \hat{Z}(\omega)\hat{I}(\omega)$ . *Note the dependence on  $\omega$ , the driving frequency.*
  - Resistors have  $\hat{Z}_R = R$  (real impedance).
  - Inductors have inductive impedance  $\hat{Z}_L = j\omega L$ .
  - Capacitors have capacitive impedance  $\hat{Z}_C = \frac{1}{j\omega C}$ .

Impedance can be written  $\hat{Z} = R + jX$ , where the imaginary part is called the *reactance* and depends on the frequency of oscillation  $\omega$  in a circuit.

- Complex impedances combine the way resistors do:

- In series,  $\hat{Z}_{eq} = \sum_i \hat{Z}_i$ .
- In parallel,  $\frac{1}{\hat{Z}_{eq}} = \sum_i \frac{1}{\hat{Z}_i}$ .