

## WUN2K FOR LECTURE 7

These are notes summarizing the main concepts you need to understand and be able to apply.

- **Power in AC circuits:** power dissipated is  $P(t) = I(t)V(t)$ . One cannot use the complex versions of current and voltage directly in this expression (because the physical quantities are real; the use of complex numbers to represent them is predicated on superposition, for linear equations). However the time average of sinusoidal signals is  $P_{\text{avg}} = \frac{1}{2}V_0I_0 \cos \phi$ , where  $\phi$  is the phase angle between current and voltage. This can also be written  $P_{\text{avg}} = \frac{1}{2}\Re(\hat{V}^*\hat{I}) = \frac{1}{2}\Re(\hat{V}\hat{I}^*)$ .
  - The *RMS* (root-mean-square) averaged power is conventionally used for AC circuits:  $V_{\text{RMS}} = \frac{V_0}{\sqrt{2}}$  and  $I_{\text{RMS}} = \frac{I_0}{\sqrt{2}}$ .
- **Transformers:** these are devices with coils typically wrapped around a core of magnetic material which transform AC voltage amplitudes.
  - The relationship between  $V_1$  and  $V_2$  is  $V_2 = \left(\frac{n_2}{n_1}\right) V_1$ , where  $n_1$  and  $n_2$  are the number of turns on each side.
  - The current relationship is  $I_2 = \left(\frac{n_1}{n_2}\right) I_1$ .
  - Transformers are used to “step up” voltages for transmission over long distances (currents are smaller so  $I^2R$  losses are smaller), and then step then down for safe use.
  - Transformers are also used for *impedance matching*: a load  $R_L$  separated from a sinusoidally driving source by a transformer will “see” an effective load impedance  $R_{\text{eff}} = \left(\frac{n_1}{n_2}\right)^2 R_L$ . The turn ratio can be chosen for maximum power transmission, which occurs when load impedance equals source output impedance.

- The basic concept of Fourier analysis, very useful for signal processing, is that any real periodic function  $f(t)$  can be written as a sum of sinusoidal terms with frequencies that are integer multiples of the fundamental frequency,  $\omega_1 = \frac{2\pi}{T}$ . We can write  $f(t) = \sum_{n=-\infty}^{\infty} \hat{c}_n e^{j\omega_n t}$ , where the Fourier coefficients are given by  $\hat{c}_n = \frac{1}{T} \int_{t'}^{t'+T} f(t) e^{-j\omega_n t} dt$ . A linear transfer function  $\hat{H}(j\omega)$  acts on each component of a signal; then one can sum the components to get the transformed signal. In general, a frequency-dependent transfer function will change the *shape* of an input signal.