

WUN2K FOR LECTURE 8

These are notes summarizing the main concepts you need to understand and be able to apply.

- The basic concept of Fourier analysis, very useful for signal processing, is that any periodic function $f(t)$ can be written as a sum of sinusoidal terms with frequencies that are integer multiples of the fundamental frequency, $\omega_1 = \frac{2\pi}{T}$. A useful way of writing this is as follows: $f(t) = a_0 + 2 \sum_{n=1}^{\infty} [a_n \cos(n\omega_1 t) - b_n \sin(n\omega_1 t)]$, where the Fourier coefficients are given by $a_n = \frac{1}{T} \int_{t'}^{t'+T} f(t) \cos(n\omega_1 t) dt$ (even contributions) and $b_n = -\frac{1}{T} \int_{t'}^{t'+T} f(t) \sin(n\omega_1 t) dt$ (odd contributions). (Note the integration is over one cycle.) A linear transfer function $\hat{H}(j\omega)$ acts on each component of a signal; then one can sum the components to get the transformed signal. In general, a frequency-dependent transfer function will change the *shape* of an input signal.
- An *amplifier* has a transfer function $\hat{A}(j\omega)$, $\hat{V}_{\text{out}}(j\omega) = \hat{A}(j\omega)\hat{V}_{\text{in}}(j\omega)$. For $|\hat{A}| > 1$ (in which case power is added to a circuit) this is referred to as “gain”.
- Common terminology used to refer to amplitude changes for filters or amplifiers:
 - Decibels are defined as $\text{dB} = 20 \log_{10}(\frac{|V_2|}{|V_1|})$.
 - For $|H(j\omega)| \sim \omega^n$, this is $\text{dB} = n20 \log_{10}(\frac{\omega_2}{\omega_1})$.
 - For an “octave” $\omega_2 = 2\omega_1$; for a “decade” $\omega_2 = 10\omega_1$. This gives 6.02n dB/octave and 20n dB/decade of frequency.
- *Filters* are networks with transfer functions that reduce some ranges of frequency but pass others.

- A *low-pass filter*, implemented simply by a resistor R in series with a capacitor C such that input is across both and output is across the capacitor, has the following properties:
 - * The transfer function is $\hat{H}(j\omega) = \frac{1}{1+j\omega RC}$.
 - * The *corner frequency* is $\omega_c = \frac{1}{RC}$. At this frequency, the response changes.
 - * For $\omega \ll \omega_C$, $H_{\text{low}} \sim 1$ (low frequencies are passed).
 - * For $\omega \gg \omega_C$, $H_{\text{high}} \sim \frac{1}{\omega RC}$ (high frequencies are attenuated).
 - * For $\omega \gg \omega_C$, the network acts as an approximate integrator (an ideal integrator has $H_I = \frac{1}{j\omega}$).
- A *high-pass filter*, implemented simply by a resistor R in series with a capacitor C such that input is across both and output is across the resistor, has the following properties:
 - * The transfer function is $\hat{H}(j\omega) = \frac{j\omega RC}{1+j\omega RC}$.
 - * The *corner frequency* is $\omega_c = \frac{1}{RC}$. At this frequency, the response changes.
 - * For $\omega \ll \omega_C$, $H_{\text{low}} \sim j\omega RC$ (low frequencies are attenuated).
 - * For $\omega \gg \omega_C$, $H_{\text{high}} \sim 1$ (high frequencies are passed).
 - * For $\omega \ll \omega_C$, the network acts as an approximate differentiator (an ideal differentiator has $H_D = j\omega$).