

Duke University
Department of Physics

Physics 271

Spring Term 2017

PRACTICE MIDTERM

I will abide by the Duke Community Standard. Name: _____

This is a closed book exam, with one side of one page cheat sheet allowed. Calculators are allowed, but only for basic calculations: you may not use special memory, graphing etc. functions. You must always show your work for credit; all answers must be justified. **You must hand in your cheat sheet with your test.**

Problem 1: (10 points)


Using only capacitors and resistors, make a sketch of a two-pole band-pass filter. Roughly sketch the resulting Bode plot, labeling the slopes of any lines. Don't use specific values for R and C but indicate relative sizes of them.

Problem 2: (10 points)

Design a diode clipper circuit that limits the output to no more than +2.3 V and -1.6 V. Sketch the output for a 100 Hz sine wave with 6 V amplitude, and for a 50 Hz square wave with 2 V amplitude.

Problem 3: (10 points)

Determine the gain of the given amplifier circuit, assuming that the amplifier's open-loop DC gain is A .

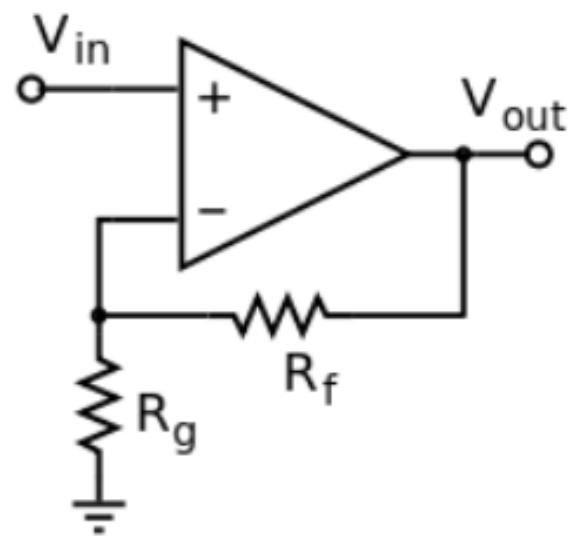


Problem 4: (10 points)

Determine the locations of the poles and zeroes of the transfer function $\hat{H}(\omega) = \frac{\omega-3}{\omega^2-4j\omega-13}$. Express your answers in the form of values of \hat{s} , and indicate their positions (in standard notation) on the complex frequency plane.

Problem 5: (20 points)


For the given circuit

- a. Determine the Thevenin resistance R_T .
- b. Find the Norton equivalent current I_N .
- c. Find the Thevenin equivalent voltage V_T .

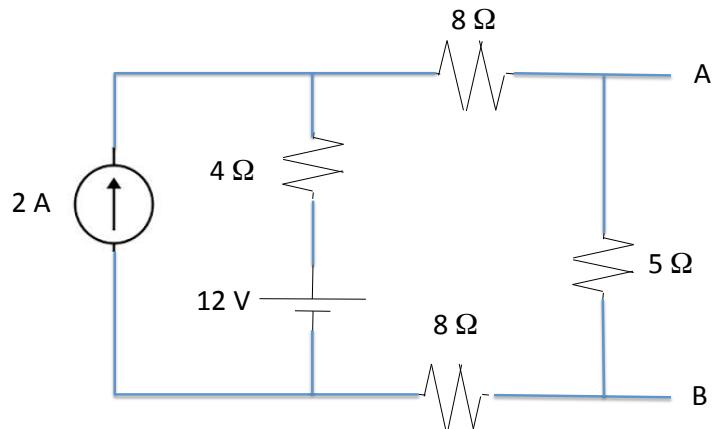


Problem 6: (20 points)

For the given circuit, show that the maximum power will be dissipated in R_{load} if $R = R_{\text{load}}$. (This is known as impedance matching, and is a useful result.)

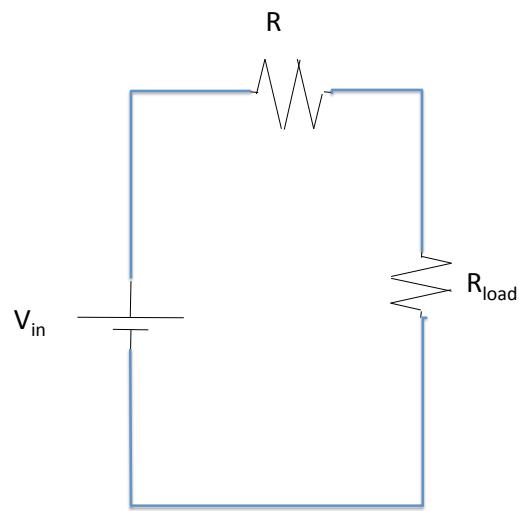

Problem 7: (25 points)

For the given filter

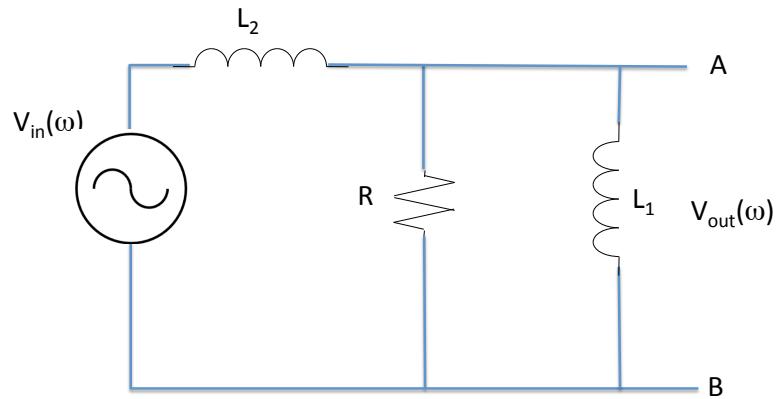

- a. What is $\hat{H}(\omega)$? Answer in terms of L_1 , L_2 , R and ω .
- b. Is this a low-pass, high-pass, band-pass or band-rejection filter? Explain. Sketch the Bode plot.
- c. Determine the corner frequency or frequencies.
- d. Determine the values of the zeroes and poles and sketch them on the complex frequency plane.
- e. Write down $|\hat{H}(\omega)|$ using the results of part d.