

Homework #10 Solutions

5.1) a) The V_{gs} voltages range for large I_d at $V_{gs} = 0V$
to zero I_d at $V_{gs} = -2.5V$

This corresponds to JFET operation

b) $V_{gs}(V)$ $I_d(sat)(mA)$ $\sqrt{I_d(sat)}(mA)^{1/2}$

0	9	3
-0.5	6.25	2.5
-1.0	4	2
-1.5	2.25	1.5
-2.0	1	1
-2.5	0.25	0.5

c) Slope of $\sqrt{I_d(sat)}$ vs. V_{gs} : $-1 \sqrt{mA}/V$
Intercept : $3 \sqrt{mA}$ @ $V_{gs} = 0$

Model
equations

$$I_d(sat) = K(V_{gs} - V_t)^2$$

$$\sqrt{I_d(sat)} = \sqrt{K}(V_{gs} - V_t)$$

$$\text{Intercept: } V_t = -3V$$


$$\sqrt{K} = 1 \sqrt{mA}/V$$

$$\Rightarrow K = 1 \text{ mA}/V^2$$

```
In [*]: import numpy as np
import matplotlib.pyplot as plt
plt.xlabel('Vgs')
plt.ylabel('Sqrt Id sat')
plt.plot([0,-0.5,-1.0,-1.5,-2.0,-2.5], np.sqrt([9.,6.25,4.,2.25,1.,0.25]), 'ro')
plt.axis([-3., 0, 0, 3.5])
plt.show()
```


```
In [*]:
```

```
In [ ]:
```

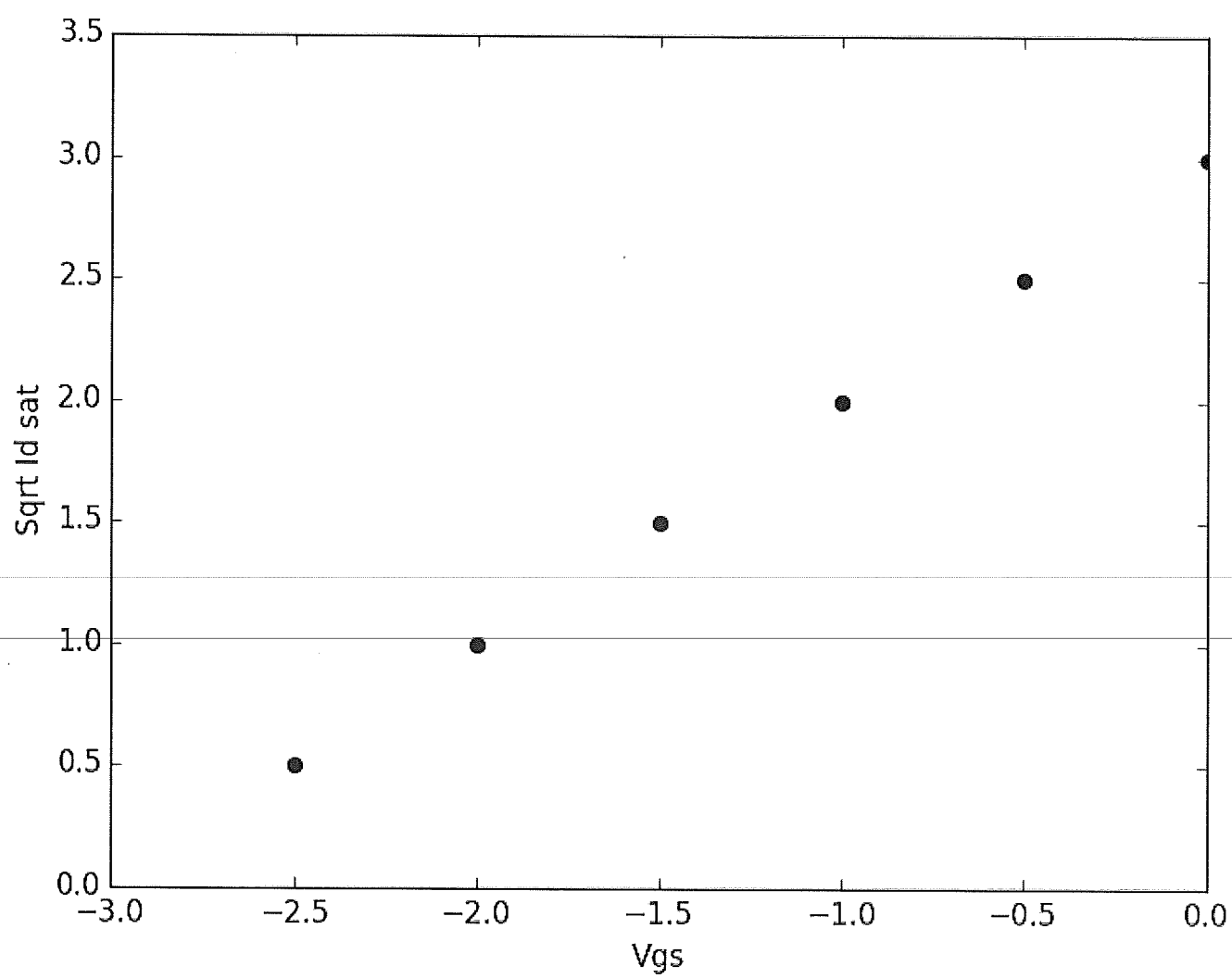

5.2) Operating Point (V_{gs} , I_d , V_{ds})

DC bias circuit

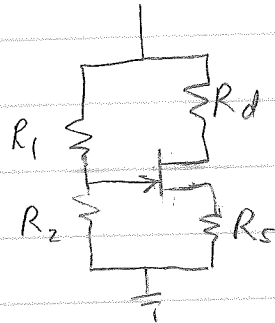

$$V_{dd} = 15V$$

$$R_1 = 1M\Omega$$

$$R_2 = 100k\Omega$$

$$R_d = 3000\Omega$$

$$R_s = 1000\Omega$$

$$V_t = -3V$$

$$K = 1mA/V^2$$

First find V_{gs} from the quadratic

$$K(V_{gs} - V_t)^2 = \frac{V_g - V_{gs}}{R_s} \quad (\text{see attachment})$$

$$V_{gs} = \underline{\underline{-1.35V}}$$

$$I_d = \frac{V_g - V_{gs}}{R_s} = \underline{\underline{2.71mA}}$$

$$V_{ds} = V_{dd} - I_d(R_s + R_d) = \underline{\underline{4.14V}}$$

In[60]:= **Ans = Solve**[$K (V_{gs} - V_t)^2 == ((V_{dd} R_2 / (R_1 + R_2)) - V_{gs}) / R_s$, V_{gs}]

$$\text{Out[60]} = \left\{ \left\{ V_{gs} \rightarrow \frac{-\frac{1}{R_s} + 2 K V_t - \frac{\sqrt{R_1 + R_2 + 4 K R_2 R_s V_{dd} - 4 K R_1 R_s V_t - 4 K R_2 R_s V_t}}{\sqrt{R_1 R_s^2 + R_2 R_s^2}}}{2 K}, \right. \right. \\ \left. \left. \left\{ V_{gs} \rightarrow \frac{-\frac{1}{R_s} + 2 K V_t + \frac{\sqrt{R_1 + R_2 + 4 K R_2 R_s V_{dd} - 4 K R_1 R_s V_t - 4 K R_2 R_s V_t}}{\sqrt{R_1 R_s^2 + R_2 R_s^2}}}{2 K} \right\} \right\}$$

In[61]:= **Ans /. Vdd -> 15 /. R1 -> 10^6 /. R2 -> 10^5 /. Rd -> 3000 /. Rs -> 1000. /. Vt -> -3 /. K -> 10^(-3)**

Out[61]= **{{Vgs -> -5.64794}, {Vgs -> -1.35206}}** *→ pick this solution since can't have $V_{gs} < V_t$*

In[62]:= **Vg = Vdd R2 / (R1 + R2);**

In[63]:= **Id = (Vg - Vgs) / Rs /. Ans[[2]] /. Vt -> -3 /. K -> 10^(-3) /. Vdd -> 15 /. R1 -> 10^6 /. R2 -> 10^5 /. Rd -> 3000 /. Rs -> 1000.**

Out[63]= **0.0027157**

In[64]:= **Vds = Vdd - Id (Rs + Rd) /. Vdd -> 15 /. Rd -> 3000 /. Rs -> 1000.**

Out[64]= **4.13721**

In[65]=


$$5.3) \quad g_m = 2K(V_{gs} - V_t)$$

$$i_D = 2(1)(-1.35 - (-3))$$

$$g_m = \underline{3.3 \times 10^{-3} \text{ A/V}}$$

In the saturation regime, the slope of I_D vs V_{gs} is zero, so we take $r_{out} \rightarrow \infty$

5.4) Common source amplifier

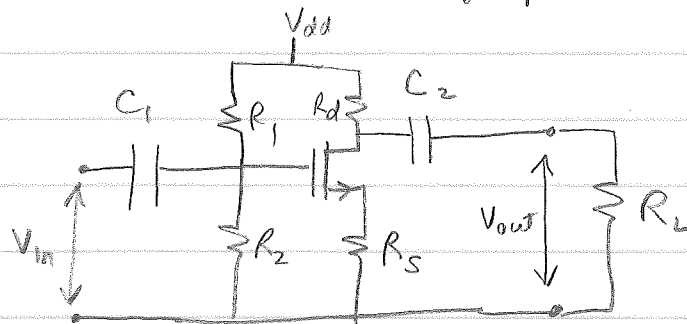

$$R_L = 10 \text{ k}\Omega$$

$$g_m = 3.3 \times 10^{-3} \frac{\text{A}}{\text{V}}$$

$$R_S = 1 \text{ k}\Omega$$

$$R_d = 3 \text{ k}\Omega$$

Voltage gain $a = \frac{-g_m R_L'}{1 + g_m R_S}$

$$R_L' = \frac{R_d R_L}{R_d + R_L} = \frac{(3)(10)}{3 + 10} = 2.31 \text{ k}\Omega$$

$$a = \frac{-(3.3 \times 10^{-3})(2.31 \times 10^3)}{1 + (3.3 \times 10^{-3})(1000)} = \underline{\underline{-1.77}}$$


Current gain $g = \frac{-g_m}{1 + g_m R_S} \left(\frac{R_d R_G}{R_d + R_L} \right)$

$$R_G = R_1 \parallel R_2 = \frac{(1)(0.1)}{1.1} = 90.9 \text{ k}\Omega$$


$$g = \frac{-(3.3 \times 10^{-3})}{(1 + (3.3 \times 10^{-3})(1000))} \left(\frac{3000 \cdot 90.9 \times 10^3}{3000 + 10000} \right)$$

$$g = \underline{\underline{-16.1}}$$

5.5) Common drain amplifier

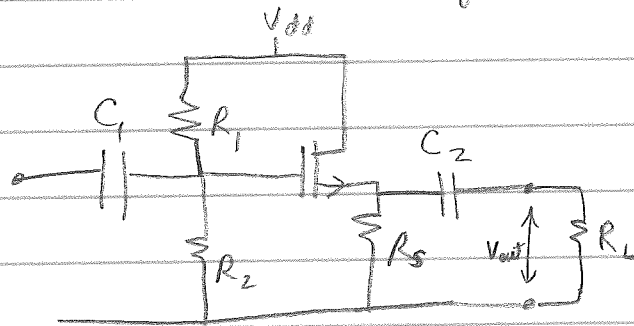

Derive: g , Z_{in} , Z_{out}

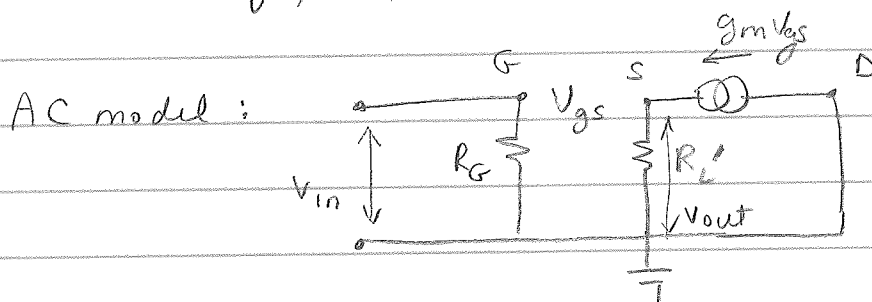

$$R_G = R_1 \parallel R_2$$

$$R_L' = R_S \parallel R_L$$

$$g = \frac{i_{out}}{v_{in}} \quad i_{in} = \frac{v_{in}}{R_G}$$

$$i_{out} = \frac{v_{out}}{R_L} \Rightarrow \frac{i_{out}}{i_{in}} = a \frac{R_G}{R_L}$$

$$a = \frac{v_{out}}{v_{in}}$$

$$v_{out} = (g_m v_{gs}) R_L'$$

$$v_{in} - v_{gs} - i_{out} R_L' = 0 \Rightarrow v_{in} = v_{gs} + g_m v_{gs} R_L'$$

$$a = \frac{g_m v_{gs} R_L'}{v_{gs} + g_m v_{gs} R_L'} = \frac{g_m R_L'}{1 + g_m R_L'}$$

Current gain

$$g = \frac{g_m R_L'}{1 + g_m R_L'} \frac{R_L}{R_G} = \frac{g_m \left(\frac{R_S R_L}{R_S + R_L} \right) \frac{R_G}{R_L}}{1 + g_m R_L'} = \frac{g_m}{1 + g_m R_L'} \frac{R_S R_G}{R_S + R_L}$$

as required

Input impedance

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{in}}{V_{in}/R_G} = \underline{\underline{R_G}}$$

$$R_L' \rightarrow R_S \\ \text{for } R_L \rightarrow \infty$$

$$Z_{out} = \frac{V_{out}(R_L \rightarrow \infty)}{I_{out}(R_L \rightarrow 0)} = \frac{g_m V_{gs} R_S}{g_m V_{gs}} = \underline{\underline{R_S}}$$

$$R_L' \rightarrow R_L \\ \text{for } R_L \rightarrow \infty$$