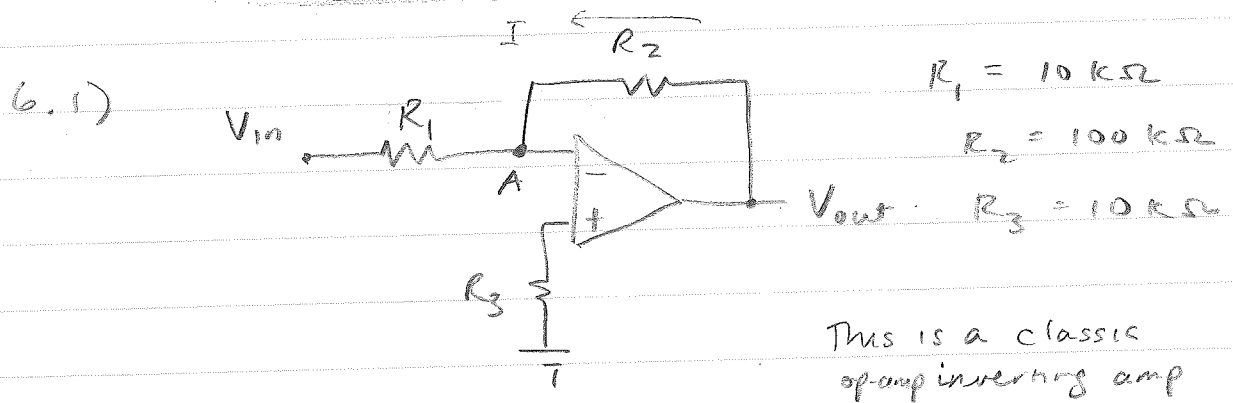


①

Homework #11 Solution



Use ideal op-amp rules.

No current drawn through R_3

$$\Rightarrow V_A = V_+ = V_- = 0$$

$$\frac{V_{out} - V_A}{R_2} = -\frac{V_{in}}{R_1}$$


$$\Rightarrow \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} = -10$$

$$V_{out} = \underline{\underline{-10 V_{in}}}$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{I_{in} R_1}{I_{in}} = R_1 = \underline{\underline{10 \text{ k}\Omega}}$$

(2)

(6.2)

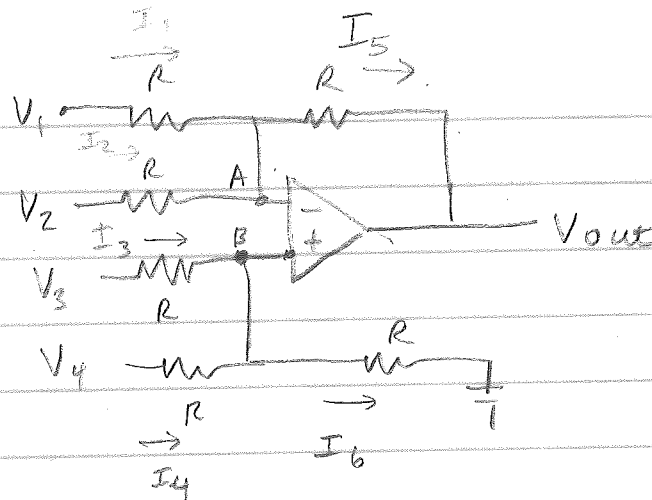

Inputs of op-amp draw no current

$$I_5 = I_1 + I_2$$

$$I_6 = I_3 + I_4$$

$$V_A = V_B$$

$$\frac{V_B}{R} = I_6 = \frac{I_3}{R} + \frac{I_4}{R} = \frac{V_3 - V_B}{R} + \frac{V_4 - V_B}{R}$$

$$V_B = V_3 - V_B + V_4 - V_B$$

$$3V_B = V_3 + V_4$$

$$\Rightarrow V_B = (V_3 + V_4)/3$$

$$\frac{V_A - V_{out}}{R} = \frac{V_1 - V_A}{R} + \frac{V_2 - V_A}{R}$$

$$V_A - V_{out} = V_1 + V_2 - 2V_A$$

$$\Rightarrow V_{out} = 3V_A - V_1 - V_2 = 3 \left(\frac{V_3 + V_4}{3} \right) - (V_1 + V_2)$$

$$\Rightarrow \boxed{V_{out} = (V_3 + V_4) - (V_1 + V_2)}$$

(3)

6.4) 741 op-amp with $\pm 15V$ power supplies:

$$\text{For a 741, } V_{sat}^+ \sim V_{cc}^+ - 1V = 14V$$

$$V_{sat}^- \sim V_{cc}^- + 1V = -14V$$

So maximum pp is $\sim \pm 14V$ so $\sim \underline{\underline{28V}}$
 max
 output
 swing

$$I_{max} = 25mA$$

at max current


$\Rightarrow$ min resistor it could drive is

$$R_{min} = \frac{14V}{25mA} = \underline{\underline{560\Omega}}$$

(4)



saturation $V_{sat}^+ = \pm 10V$

6.5)

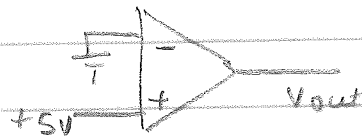
Open Loop

$$V_{out} = A_{OL}(V_{in}^+ - V_{in}^-)$$

↓
but saturated
for $\sim 5V$ inputs
 $+5V$ for $V_{in}^+ > V_{in}^-$
 $-5V$ for $V_{in}^+ < V_{in}^-$

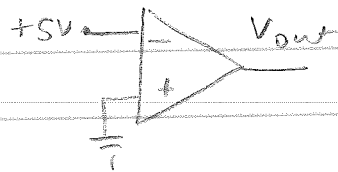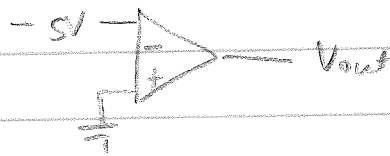This has $V_{in}^+ > V_{in}^- \Rightarrow V_{out} = \underline{\underline{+10V}}$ This has $V_{in}^+ < V_{in}^- \Rightarrow V_{out} = \underline{\underline{-10V}}$ This has $V_{in}^+ > V_{in}^-$

$$\Rightarrow V_{out} = \underline{\underline{+10V}}$$

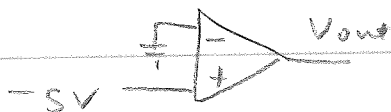
this has $V_{in}^+ < V_{in}^-$

$$\Rightarrow V_{out} = \underline{\underline{-10V}}$$

(5)

6.6) Inverting amp w/ $R_1 = 5 \text{ k}\Omega$

$$\text{Gain} = -75$$

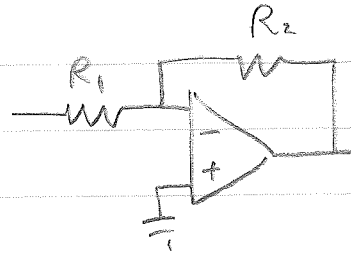

$$\text{Gain} = -\frac{R_2}{R_1} = -75$$

$$\Rightarrow R_2 = (5 \text{ k}\Omega)(75) = \underline{\underline{375 \text{ k}\Omega}}$$


$$6.7) V_{CC}^{\pm} = \pm 12 \text{ V}$$

$$V_{\text{sat}}^{\pm} \sim \pm 11 \text{ V}$$

maximum output voltage

$$\text{So when } V_{\text{in}} = \frac{11 \text{ V}}{75} = \underline{\underline{147 \text{ mV}}}$$

(6)

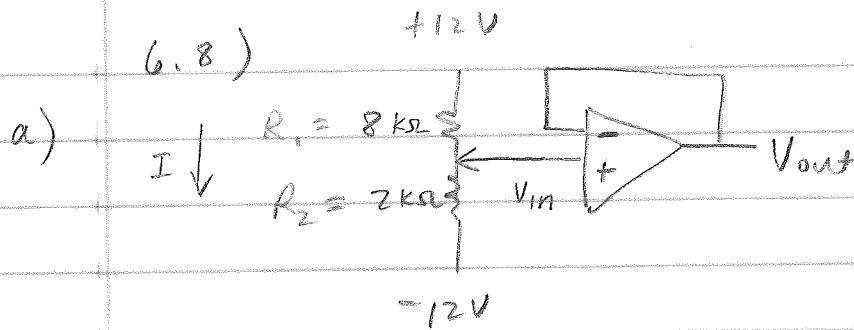

$V_{in} = V_{out}$ by ideal op-amp rule.


$$I = \frac{V_{cc} - V_{in}}{R_1} = \frac{V_{in} + V_{cc}}{R_2}$$

$$V_{in} \left(\frac{1}{R_2} + \frac{1}{R_1} \right) = \frac{V_{cc}}{R_1} - \frac{V_{cc}}{R_2}$$

$$V_{in} = V_{cc} \left(\frac{R_2 - R_1}{R_1 R_2} \right) \left(\frac{R_1 R_2}{R_2 + R_1} \right) = V_{cc} \left(\frac{R_2 - R_1}{R_2 + R_1} \right)$$

$$= 12 \left(\frac{-6k\Omega}{10k\Omega} \right) = -7.2V$$
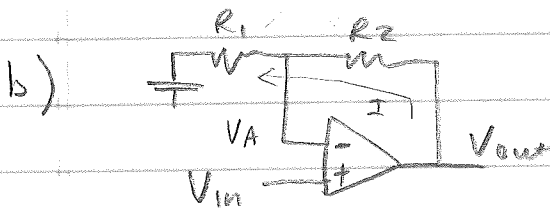
$$\Rightarrow V_{out} = \underline{\underline{-7.2V}}$$



$$V_{in} = +1V$$

$$R_1 = 1k\Omega$$


$$R_2 = 10k\Omega$$

$$V_A = V_{in} = +1V$$

$$\frac{V_{out} - V_A}{R_2} = \frac{V_A}{R_1}$$

$$V_{out} = \frac{R_2}{R_1} V_A + V_A = 10 \cdot V_A + V_A = \underline{\underline{11V}}$$

7

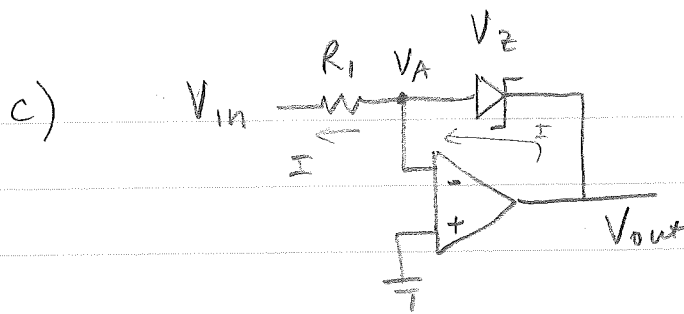

$$V_{in} = -3V$$

$$R_1 = 1k\Omega$$


$$V_Z = 6.2V$$

$$V_A = 0 \text{ (virtual ground)}$$

$V_{out} = V_Z$ so long as Zener is in breakdown mode

If $V_{in} = -3V$, $I = \frac{3V}{1k\Omega} = 3mA \rightarrow$ should be going to left through Zener,
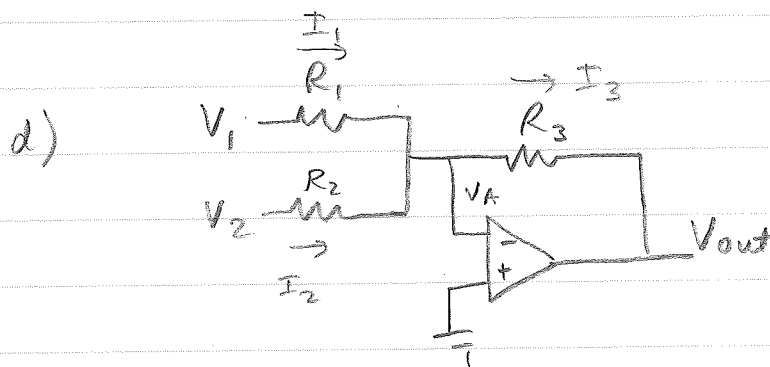
$$\Rightarrow V_{out} = V_Z = \underline{\underline{6.2V}}$$



$$R_1 = 2k\Omega$$

$$R_2 = 2k\Omega$$

$$R_3 = 1k\Omega$$

$$V_1 = 1V$$

$$V_2 = 2V$$

$$I_1 + I_2 = I_3$$

$$V_A = 0 \Rightarrow -\frac{V_{out}}{R_3} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$V_{out} = -1k\Omega \left(\frac{1V}{2k\Omega} + \frac{2V}{2k\Omega} \right)$$

$$= -1(0.5 + 1)$$

$$V_{out} = \underline{\underline{-1.5V}}$$