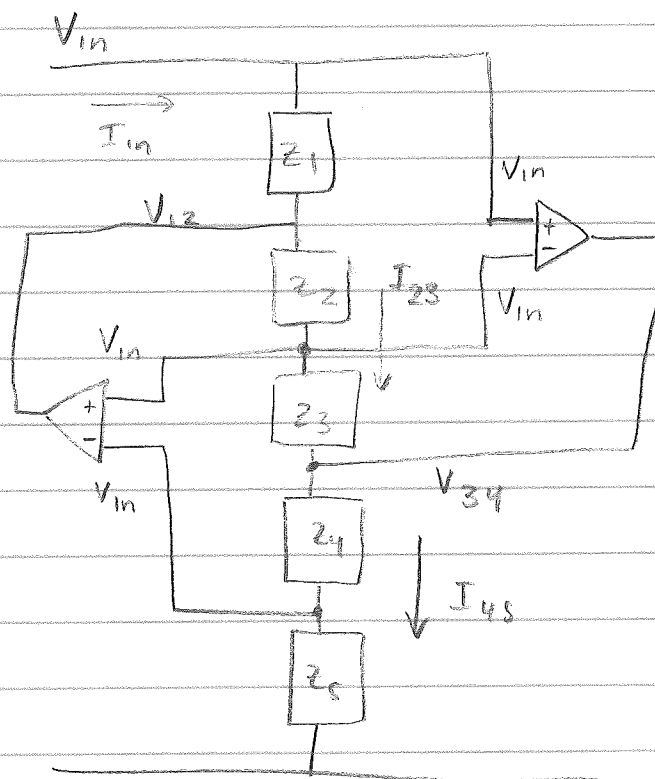


(1)

Homework #12 Solution

1) Gyrator circuit



$$I_{45} = \frac{V_{in}}{Z_5} = \frac{V_{34} - V_{in}}{Z_4}$$

$$V_{34} = V_{in} \left(\frac{Z_4}{Z_5} + 1 \right)$$

$$I_{23} = \frac{V_{in} - V_{34}}{Z_3}$$

$$= \frac{V_{in}}{Z_3} \left[1 - \frac{Z_4}{Z_5} - 1 \right]$$

$$I_{23} = V_{in} \left(\frac{-Z_4}{Z_3 Z_5} \right)$$

$$I_{23} = \frac{V_{12} - V_{in}}{Z_2} \Rightarrow V_{12} = I_{23} Z_2 + V_{in}$$

$$V_{12} = V_{in} \left(\frac{-Z_2 Z_4}{Z_3 Z_5} + 1 \right)$$

$$I_{in} = \frac{V_{in} - V_{12}}{Z_1} = \frac{V_{in}}{Z_1} \left(1 - \frac{V_{12}}{V_{in}} \right)$$

$$= \frac{V_{in}}{Z_1} \left[1 + \frac{Z_2 Z_4}{Z_3 Z_5} - 1 \right]$$

$$I_{in} = V_{in} \left(\frac{Z_2 Z_4}{Z_1 Z_3 Z_5} \right)$$


$$\Rightarrow Z_{in} = \frac{V_{in}}{I_{in}} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

To get a circuit that behaves like an inductor, choose

$$\begin{cases} z_2 = C_G & (\text{also works if } z_4 = C_G) \\ \text{all other } z\text{'s} & z_1 = z_3 = z_4 = z_5 = R_G \end{cases}$$

$$\text{Then } z_{in} = \frac{R_G^3}{\frac{1}{j\omega C_G} R_G} = j\omega \underbrace{R_G^2 C_G}_{L_{eqw}}$$

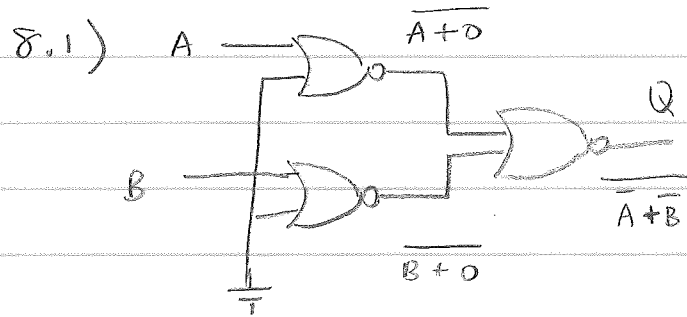Behaves like an inductive impedance $\underline{z_{in} = j\omega L_{eqw}}$



$$A+0 = A$$

$$\overline{A+0} = \overline{A}$$

Note this is $\overline{A+B} = \overline{A} \cdot \overline{B}$

Assume a logic system such that ground $\rightarrow 0$


$= A \cdot B$
by
de Morgan

A	B	$\overline{A}$	$\overline{B}$	Q
0	0	1	1	0
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1

↑
same as $A+B$

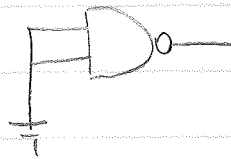
8.2) Use only NAND gates (simplify with Boolean algebra)

$$\begin{aligned}
 a) \quad & (AB) + (\bar{A}B) + (A\bar{B}) + (\bar{A}\bar{B}) \\
 &= \underbrace{(A+\bar{A})}_1 B + \underbrace{(A+\bar{A})}_1 \bar{B} \\
 &= B + \bar{B} \\
 &= 1, \text{ i.e. always true}
 \end{aligned}$$




will do the trick
 $0+0 = 1$
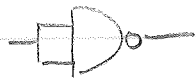
$$\begin{aligned}
 b) \quad & [(A \cdot B) + C] \cdot [(A \cdot B) + D] = (AB)(AB) + C(AB) + ABD + CD \\
 &= \underbrace{AB + C(AB) + D(AB)}_{AB} + CD \\
 &= \underbrace{AB + D(AB)}_{AB} + CD \\
 &= AB + CD
 \end{aligned}$$




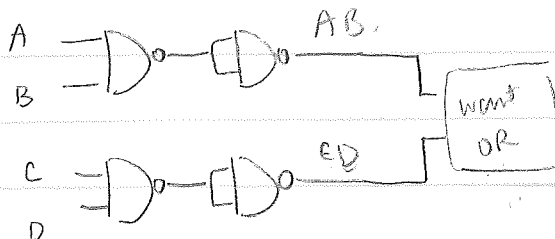is an inverter : both inputs 0 $\Rightarrow$ NAND gives 1
 both inputs 1 $\Rightarrow$ NAND gives 0




De Morgan

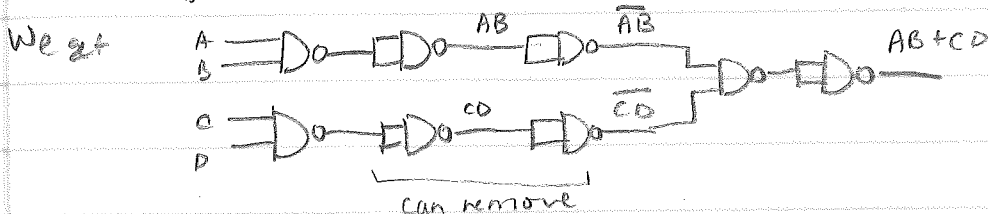
$$\begin{aligned}
 AB + CD &= \overline{\overline{AB} \cdot \overline{CD}} \\
 &\text{so can make} \\
 &\text{OR with inverters \& AND}
 \end{aligned}$$




Simplified:

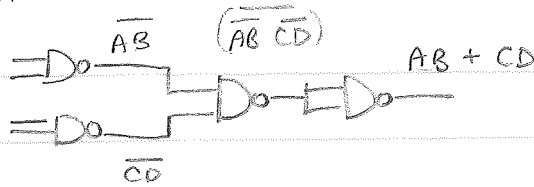
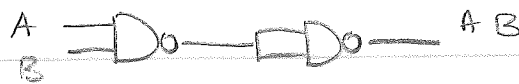
$$c) [(\bar{A}B)(AB)] + (AB) = (\bar{A}B + 1)AB = AB \quad , \text{ just AND}$$



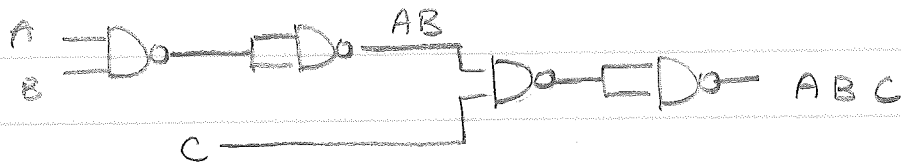
$$d) \underbrace{(1+B)}_1 \cdot (ABC) = ABC$$




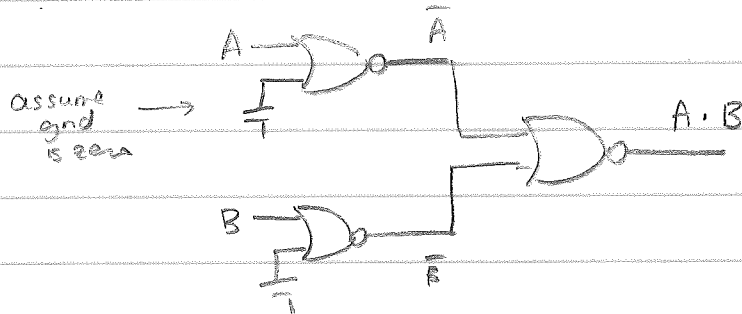8.3) Using only NOR : use Boolean rules


$$\text{AND: } A \cdot B = \overline{\overline{A + B}} = \overline{\overline{A + 0} + \overline{B + 0}}$$


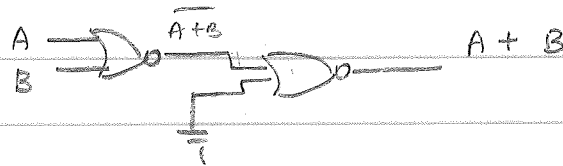
$$\text{OR } A + B = \overline{\overline{A + B}} = \overline{(\overline{A + B}) + 0}$$


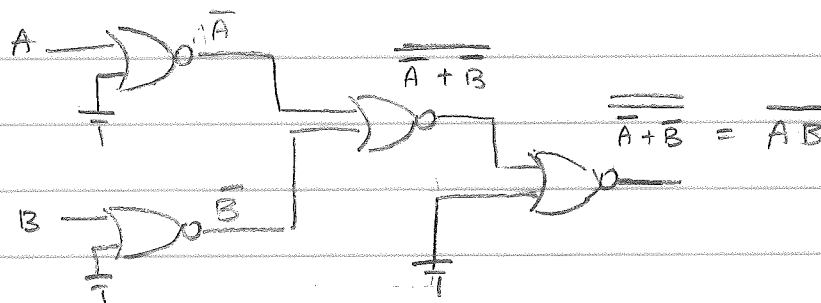
$$\text{NAND } \overline{A \cdot B} = \overline{\overline{A + B}} = \overline{\overline{A + B}} = \overline{(\overline{A + 0} + \overline{B + 0}) + 0}$$





XOR

$$A \oplus B = A\bar{B} + \bar{A}B$$

$$= \overline{\bar{A} + B} + \overline{A + \bar{B}}$$
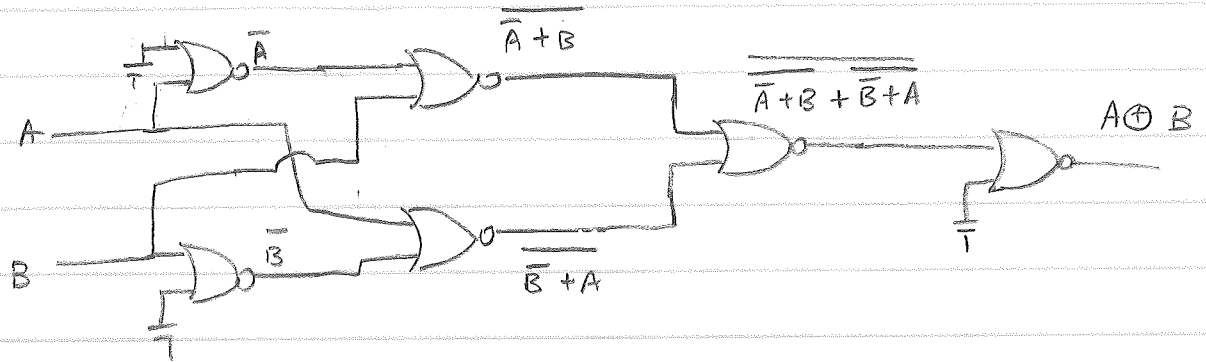
$$= \overline{\bar{A} + B} + \overline{A + \bar{B}}$$



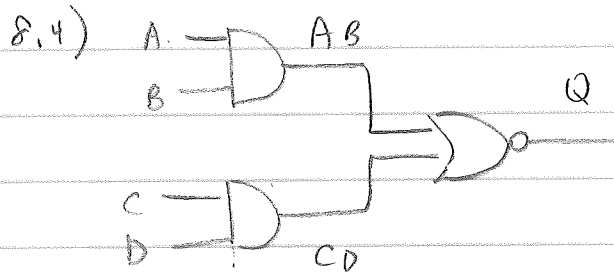

(16 possible
input
combinations)

A	B	C	D	AB	CD	Q
0	0	0	0	0	0	1
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	0	1
0	1	1	0	0	0	1
0	1	1	1	0	1	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	1	0