

Homework #13

1) Full adder from class : adding 2 2-bit numbers

$$\begin{array}{r}
 C_2 C_1 \\
 X_1 X_0 \\
 Y_1 Y_0 \\
 \hline
 C_2 Z_1 Z_0 \\
 \downarrow \\
 C_2, \text{ carry bit}
 \end{array}$$

Truth table

	C_1	X_1	Y_1	C_2	Z_1
	0	0	0	0	0
*	0	0	1	0	1
*	0	1	0	0	1
	0	1	1	1	0
*	1	0	0	0	1
	1	0	1	1	0
	1	1	0	1	0
*	1	1	1	1	1

For Z_1 true : make Boolean statement for the starred rows

$$Z_1 = \bar{C}_1 (\underbrace{\bar{X}_1 Y_1 + X_1 \bar{Y}_1}_{X_1 \oplus Y_1}) + C_1 (\bar{X}_1 \bar{Y}_1 + X_1 Y_1)$$

$$= \bar{C}_1 (X_1 \oplus Y_1) + C_1 (\bar{X}_1 \bar{Y}_1 + X_1 Y_1)$$

$$A + 0 = A$$

②

$$\text{2nd term: } \bar{X}_1 \bar{Y}_1 + X_1 Y_1 = \bar{X}_1 \bar{Y}_1 + X_1 Y_1 + \overbrace{X_1 \bar{X}_1}^0 + \overbrace{Y_1 \bar{Y}_1}^0$$

$$= (\bar{X}_1 + \bar{Y}_1)(\bar{X}_1 + Y_1)$$

↓ dem.

$$= (\overline{\bar{X}_1 Y_1}) \cdot (\overline{X_1 \bar{Y}_1})$$

↓ dem

$$= \overline{\bar{X}_1 Y_1 + X_1 \bar{Y}_1}$$

$$= \overline{X_1 \oplus Y_1}$$

$$\Rightarrow z_1 = \bar{C}_1 (X_1 \oplus Y_1) + C_1 (\overline{X_1 \oplus Y_1})$$

$$u \equiv X_1 \oplus Y_1$$

$$\Rightarrow z_1 = \bar{C}_1 u + C_1 \bar{u}$$

$$z_1 = C_1 \oplus u$$

$$\Rightarrow \boxed{z_1 = C_1 \oplus (X_1 \oplus Y_1)} \text{ as required.}$$


8.6) Want alarm system to light an LED
when any of 5 doors are open

Open door $\rightarrow$ high

Assume LED turns on when high voltage level across it


Use only 2-input logic gates

$$\text{Want: } A+B+C+D+E = 1$$

 

8.7) Make a clocked flip-flop
w/ functionality as

Eggleston Fig 8.31

 

NAND:

0	0	1
0	1	1
1	0	1
1	1	0

NAND output goes high if either input low

$Q \text{ low} \Rightarrow \bar{Q} \text{ high}$

$\bar{Q} \text{ low} \Rightarrow Q \text{ high}$

Behavior of basic flip flop on the right	S	S'	R'	Q	$\bar{Q}$
		0	0	1	1
		0	1	1	0
		1	0	0	1
		1	1	no change	
				$\left. \begin{array}{l} \text{if } Q=0, \bar{Q}=1 \\ \text{if } \bar{Q}=0, Q=1 \end{array} \right\} \text{ (bistable)}$	

Now behavior with S, C, R added on the left: if C is low
S' and R' are both high, and there is no change at Q, $\bar{Q}$. If C is high, S and R are inverted


Replacing NANDs with NORs:

With C high	S	R	S'	R'	Q	$\bar{Q}$
	0	0	1	1	no change	
	0	1	1	0	0	1
	1	0	0	1	1	0
	1	1	0	0	unstable	

NOR

0	0	1
0	1	0
1	0	0
1	1	0

NOR output goes low if either input high

 

So as for the NAND gate FF,

$Q \text{ high} \Rightarrow \bar{Q} \text{ low}$

$\bar{Q} \text{ high} \Rightarrow Q \text{ low}$

Also bistable

(5)

So we have for the right hand FF

S'	R'	Q	$\bar{Q}$
0	0	no change	
0	1	1	0
1	0	0	1
1	1	0	0 $\rightarrow$ avoid, unstable

Now adding S, C, R on the left:

if C is high, S' and R' go low,
so no change at the output

If C is low,

S	R	S'	R'	Q	$\bar{Q}$
0	0	1	1	unstable	
0	1	1	0	0	1
1	0	0	1	1	0
1	1	0	0	no change	

So we get the same behavior as
the version with NANDs for $(S, R) \rightarrow (Q, \bar{Q})$

(different unstable condition)

To get the same behavior for C , use an inverter

Overall
circuit
w/ 5
NOR gates

