

Homework #1 Solutions

1.1) Nichrome wire $d = 1 \text{ mm}$, $L = 1 \text{ m}$

$$R = \frac{\rho L}{A}, \quad \rho = 100 \times 10^{-8} \Omega \text{ m (Table 1.2)}$$

$$= \frac{(100 \times 10^{-8})(1)}{\pi (0.5 \times 10^{-3})^2} \Omega$$

$$R = \underline{\underline{1.27 \Omega}}$$

1.2) Maximum allowable current through $R = 10 \text{ k}\Omega$,
for $P = 10 \text{ W}$ //

Power dissipated by an ohmic resistor

$$P = I^2 R$$

$$I_{\text{max}} = \sqrt{P/R} = \sqrt{10 / (10 \times 10^3)} = \underline{\underline{0.032 \text{ A}}}$$

For $R = 10 \text{ k}\Omega$, $P = 0.25 \text{ W}$

$$I_{\text{max}} = \sqrt{0.25 / (10 \times 10^3)} = \underline{\underline{0.005 \text{ A}}}$$

(2)

1.3) a) $R = 100 \Omega$
 $V = 100 \text{ V}$

Ohmic resistor $V = IR$


Power is $P = IV = \frac{V^2}{R}$

$$P = \frac{(100)^2}{100} = \underline{\underline{100 \text{ W}}}$$

b) For $R = 100 \text{ k}\Omega$

$$P = \frac{(100)^2}{10^5} = \underline{\underline{0.1 \text{ W}}}$$


1.4)

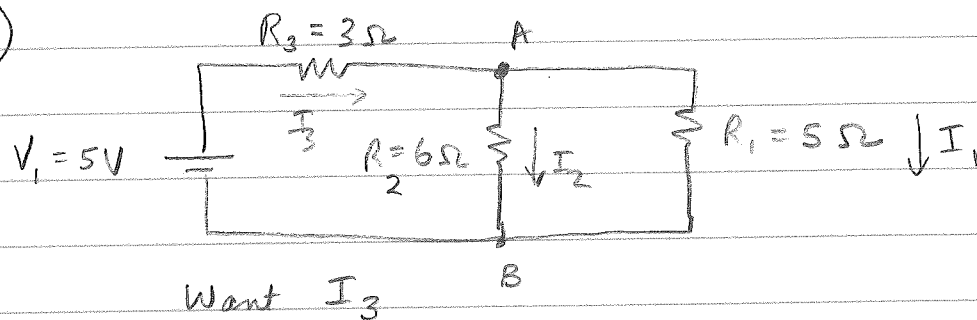

Apply Kirchhoff:

$$\left. \begin{aligned} I_3 &= I_2 + I_1 \\ V_1 - I_3 R_3 - I_2 R_2 &= 0 \\ V_1 - I_3 R_3 - I_1 R_1 &= 0 \end{aligned} \right\} \begin{array}{l} 3 \text{ eqns,} \\ 3 \text{ unknowns,} \\ \text{can solve} \end{array}$$

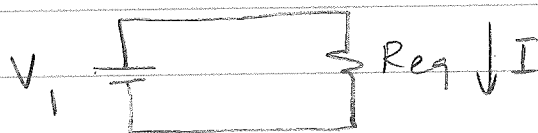But an easier way for this problem: consider as



The current through "Req" will be the same as through R_3

$$R_{eq} = R_3 + R_1 \parallel R_2 = R_3 + \frac{R_1 R_2}{R_1 + R_2} = 3 + \frac{(6)(5)}{6+5} = 5.73 \Omega$$

$$I = V_1 / R_{eq} = 5\text{V} / 5.73 \Omega = \underline{\underline{0.873 \text{ A}}}$$

1.5) Using voltage divider equation,
voltage at point A is

$$V_A = \frac{R_2 \parallel R_1}{R_3 + R_2 \parallel R_1} V_1 =$$

$$R_2 \parallel R_1 = \frac{R_1 R_2}{R_1 + R_2} = \frac{(5)(6)}{5+6} = 2.727 \Omega$$


$$V_A = \frac{2.727}{2.727 + 3} (5V) = 2.38V$$

$$V_B = 0$$

$$\text{So } I_1 = V_A / R_1 = 2.38 / 5 = \underline{\underline{0.476A}}$$

$$I_2 = V_A / R_2 = 2.38 / 6 = \underline{\underline{0.397A}}$$

1.6) Voltage divider

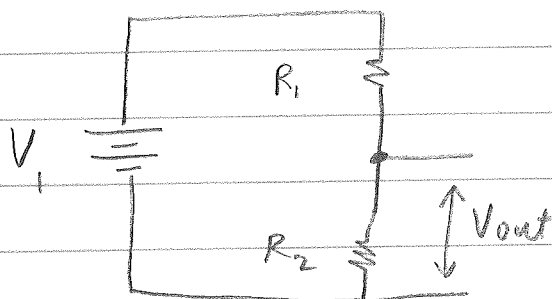


$$V_1 = 3V$$


$$R_1 = 2k\Omega$$

$$R_2 = 1k\Omega$$

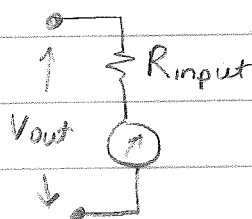Voltmeter: need to consider its internal resistance



so looks like

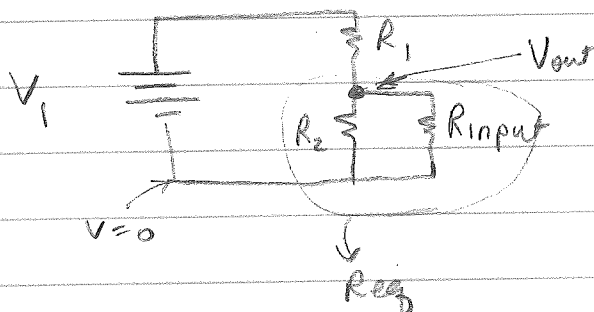

$$V_{out} = \frac{R_{eq}}{R_1 + R_{eq}} V_1$$

$$R_{eq} = R_2 \parallel R_{input}$$

$$R_{eq} = \frac{R_2 R_{input}}{R_2 + R_{input}}$$

What the meter reads:

$$V_{out} = \frac{V_1 R_2 R_{input}}{R_1 + R_2 R_{input} / (R_2 + R_{input})} = \frac{R_2 R_{input} V_1}{R_1 R_2 + R_1 R_{input} + R_2 R_{input}}$$

For $R_{input} = 100\Omega$:
$$V_{out} = \frac{(10^3)(10^2)(3)}{(2 \times 10^3)(10^3) + (2 \times 10^3)(100) + (10^3)(100)} = \underline{\underline{0.130V}}$$


Similarly for $R_{input} = 1k\Omega$, $V_{out} = \underline{\underline{0.600V}}$

$R_{input} = 50k\Omega$, $V_{out} = \underline{\underline{0.987V}}$

$R_{input} = 1M\Omega$, $V_{out} = \underline{\underline{0.999V}}$

Note that the higher the meter internal resistance, the closer V_{out} is to the value without the meter

1.7)

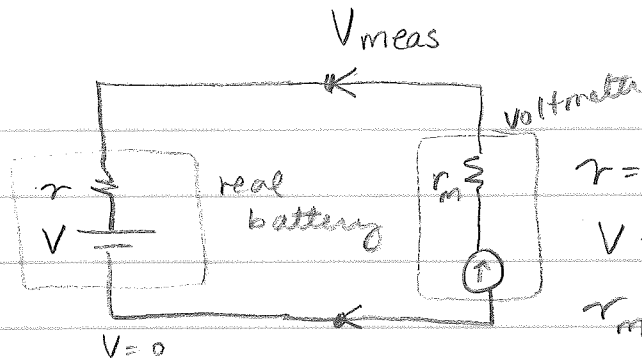

r = battery internal resistance
 V = ideal source voltage
 r_m = voltmeter internal resistance

$$r_m = 1000 \, \Omega$$

$$V = 1.5 \, \text{V}$$

$$V_{\text{meas}} = 0.9 \, \text{V}$$

Treat as voltage divider
$$V_{\text{meas}} = \frac{r_m}{r + r_m} V$$

Solve for r

$$r + r_m = r_m \frac{V}{V_{\text{meas}}}$$

$$r = r_m \frac{V}{V_{\text{meas}}} - r_m = 10^3 \left(\frac{1.5}{0.9} \right) - 10^3$$


$$r = \underline{\underline{667 \, \Omega}}$$

1.8) Same relation
$$V_{\text{meas}} = \frac{r_m}{r + r_m} V, \text{ but } r_m = 10 \times 10^6 \, \Omega$$

$$V_{\text{meas}} = \frac{10 \times 10^6}{(10 \times 10^6) + 667} \cdot 1.5 = \underline{\underline{1.499 \, \text{V}}}$$

Note: Large meter resistance $\rightarrow$ closer to "ideal" measurement

1.9)

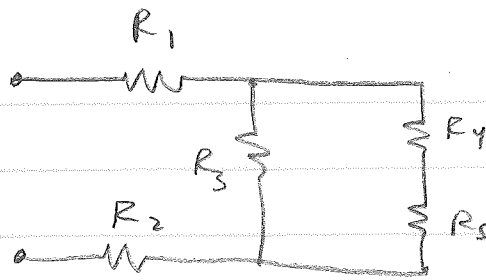

$$R_1 = 3\Omega$$

$$R_2 = 2\Omega$$


$$R_3 = 15\Omega$$

$$R_4 = 10\Omega$$

$$R_5 = 5\Omega$$

Want equivalent resistance of this network

Redraw:

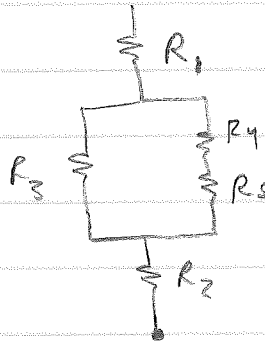

$$R_{eq} = R_1 + R_3 \parallel (R_4 + R_5) + R_2$$


$$= R_1 + \frac{R_3(R_4 + R_5)}{R_3 + R_4 + R_5} + R_2$$

$$= 3 + \frac{15(10 + 5)}{15 + 10 + 5} + 2$$

$$R_{eq} = \underline{\underline{12.5\Omega}}$$

1.10) Consider a battery across the terminals

$$V = 25 \text{ V}$$

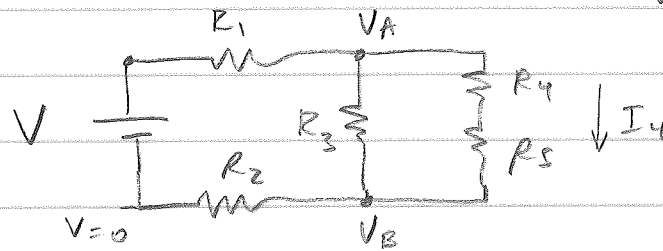

What is current in R_4 ?
(I_4)

$$I = \frac{V}{R_{eq}}$$

through whole circuit

$$I = \frac{25 \text{ V}}{12.5 \Omega} = 2 \text{ A}$$

Kirchhoff's Loop Rule

$$V - IR_1 - I_4(R_4 + R_5) - IR_2 = 0$$


Solve for I_4

$$I_4 = \frac{V - IR_1 - IR_2}{(R_4 + R_5)}$$

$$= \frac{25 - (2)(3) - 2(2)}{15}$$

$$I_4 = \underline{\underline{1 \text{ A}}}$$

1.11)

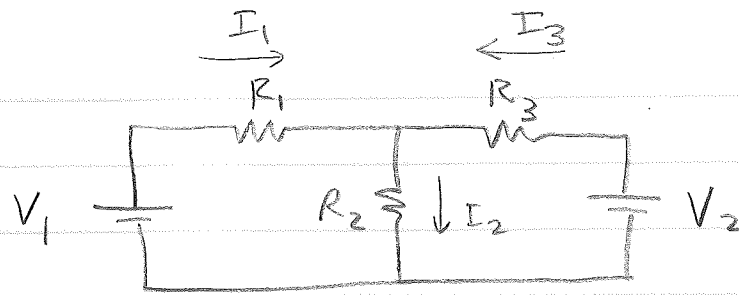

$$V_1 = 5V$$

$$V_2 = 15V$$

$$R_1 = 3\Omega$$

$$R_2 = 5\Omega$$

$$R_3 = 8\Omega$$

Want I_2, I_3

Use Kirchhoff's Rules

$$V_1 - I_1 R_1 - I_2 R_2 = 0$$

$$V_2 - I_3 R_3 - I_2 R_2 = 0$$

$$I_1 = I_2 - I_3$$

3 eqns,
3 unknowns

Solve:

$$I_3 = \frac{V_2 - I_2 R_2}{R_3}$$

$$V_1 - (I_2 - I_3) R_1 - I_2 R_2 = 0$$

$$V_1 - I_2(R_1 + R_2) + I_3 R_1 = 0$$

$$V_1 - I_2(R_1 + R_2) + \left(\frac{V_2 - I_2 R_2}{R_3}\right) R_1 = 0$$

Solve for I_2

$$V_1 - I_2 \left(R_1 + R_2 + \frac{R_2 R_1}{R_3} \right) + \frac{V_2 R_1}{R_3} = 0$$

$$I_2 = \frac{V_1 + V_2 R_1 / R_3}{(R_1 + R_2 + R_2 R_1 / R_3)} = \frac{(5 + 15 \cdot 3 / 8)}{(3 + 5 + 3 \cdot 5 / 8)} = \underline{\underline{1.076A}}$$

$$\text{Solve for } I_3 \quad I_3 = \frac{V_2 - I_2 R_2}{R_3} = \frac{15V - (1.076)(5)}{8} = \underline{\underline{1.20A}}$$