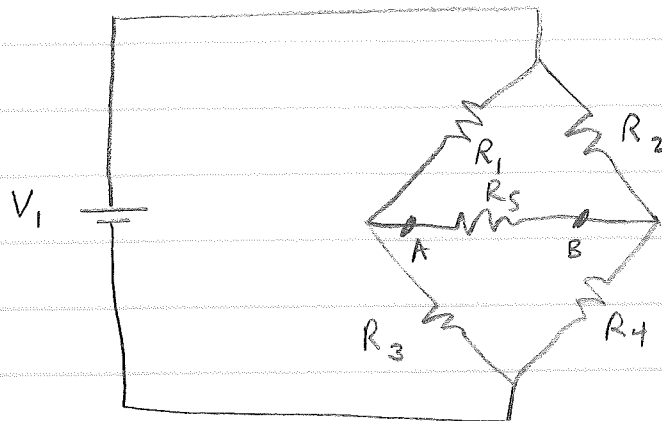


①

Homework # 2 Solutions

1.13)



$$V_1 = 10 \text{ V}$$

$$R_1 = 100 \, \Omega$$

$$R_2 = 1 \text{ k}\Omega$$

$$R_3 = 99 \, \Omega$$


$$R_4 = 1 \text{ k}\Omega$$

$$R_5 = 10 \, \Omega$$

Find V_{Th} , R_{Th} w/ R_5 removed.

This problem was done in class.

To find V_{Th} , find V_{AB} (open).

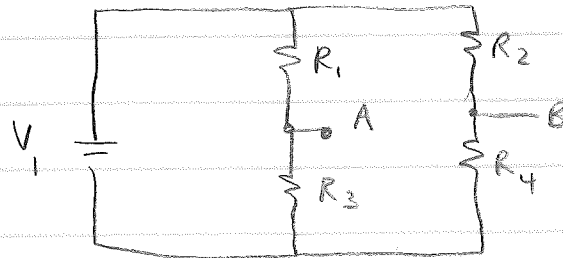

We have two voltage dividers

$$V_A = V_1 \left(\frac{R_3}{R_1 + R_3} \right) = (10) \left(\frac{99}{100 + 99} \right)$$

$$V_A = 4.97 \text{ V}$$

$$V_B = V_1 \left(\frac{R_4}{R_2 + R_4} \right) = \left(10 \cdot \frac{1000}{1000 + 1000} \right)$$



$$= 5 \text{ V}$$

$$\Rightarrow V_B - V_A = 5 - 4.97 \text{ V}$$

$$V_{Th} = V_B - V_A = \underline{\underline{0.025 \text{ V}}}$$

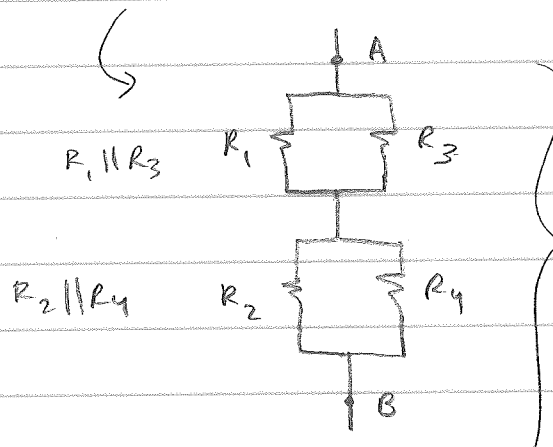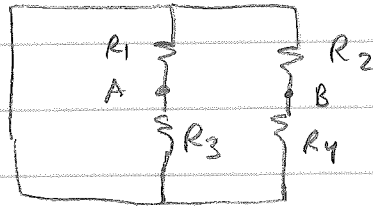(2)

Now the Thevenin resistance is the equivalent resistance with V_1 shorted




$$R_{Th} = \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4}$$

$$= \frac{(100)(99)}{100 + 99} + \frac{(1000)(1000)}{2000}$$

$$= \underline{\underline{549.7 \, \Omega}}$$


1.14) Now find current through R_5

The circuit without R_5 is equivalent to

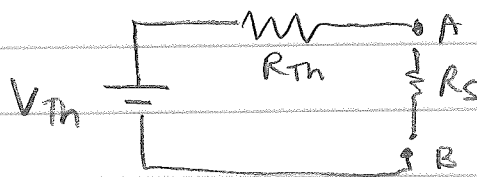

$$\text{So } I_{R_5} = \frac{V_{Th}}{R_{Th} + R_5} = \frac{0.025 \, \text{V}}{(549.7 \, \Omega + 10)} = \underline{\underline{0.049 \, \text{mA}}}$$

1.17)

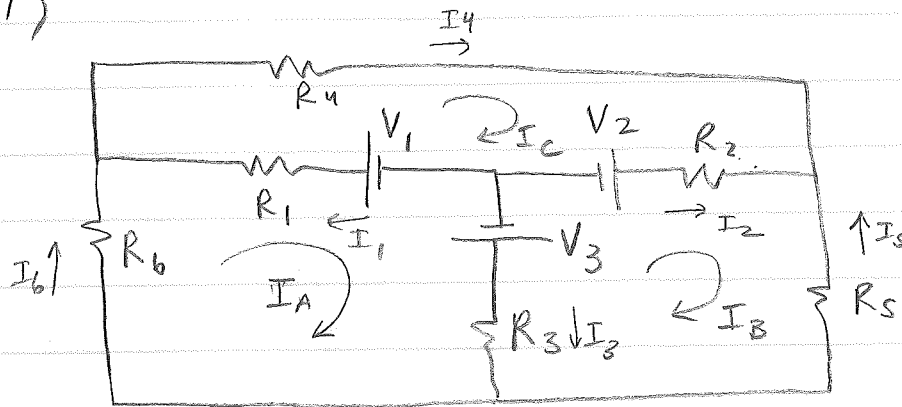

$$\begin{aligned}
 V_1 &= 5\text{ V} \\
 V_2 &= 10\text{ V} \\
 V_3 &= 15\text{ V} \\
 R_1 &= 2\ \Omega \\
 R_2 &= 4\ \Omega \\
 R_3 &= 6\ \Omega \\
 R_4 &= 7\ \Omega \\
 R_5 &= 5\ \Omega \\
 R_6 &= 3\ \Omega
 \end{aligned}$$

Use "mesh loop" method for easier algebra

Walk around each loop

$$V_3 - (I_A - I_B)R_3 - I_A R_6 - (I_A - I_C)R_1 - V_1 = 0$$

$$V_2 - (I_B - I_C)R_2 - I_B R_5 - (I_B - I_A)R_3 - V_3 = 0$$

$$V_1 - (I_C - I_A)R_1 - I_C R_4 - (I_C - I_B)R_2 - V_2 = 0$$

Rearrange : put voltages on RHS

$$(-R_3 - R_6 - R_1)I_A + R_3 I_B + R_1 I_C = V_1 - V_3$$

$$R_3 I_A + (-R_2 - R_5 - R_3)I_B + R_2 I_C = V_3 - V_2$$

$$R_1 I_A + R_2 I_B + (-R_1 - R_4 - R_2)I_C = V_2 - V_1$$

Now plug this set of simultaneous linear equations into a computer - any method OK.

See attached Mathematical notebook

Mathematica notebook for simultaneous equation solution

```
In[39]:= ClearAll["Global`*"]
```

```
In[40]:=
```

```
In[41]:= Isol =
```

```
Solve[{{(-R3 - R1 - R6) Ia + R3 Ib + R1 Ic == V1 - V3, R3 Ia + (-R2 - R5 - R3) Ib + R2 Ic == V3 - V2, R1 Ia + R2 Ib + (-R1 - R4 - R2) Ic == V2 - V1}, {Ia, Ib, Ic}] /. V1 -> 5 /. V2 -> 10 /. V3 -> 15 /. R1 -> 2 /. R2 -> 4 /. R3 -> 6 /. R4 -> 7 /. R5 -> 5 /. R6 -> 3.
```

```
Out[41]= {{Ia -> 0.810409, Ib -> -0.0855019, Ic -> -0.286245}}
```

$$I_1 = I_C - I_A = \underline{\underline{-1.1 A}}$$

$$I_2 = I_B - I_C = \underline{\underline{0.20 A}}$$


$$I_3 = I_A - I_B = \underline{\underline{0.90 A}}$$

$$I_4 = I_C = \underline{\underline{-0.29 A}}$$

$$I_5 = -I_B = \underline{\underline{0.086 A}}$$

$$I_6 = I_A = \underline{\underline{0.81 A}}$$

1.18)

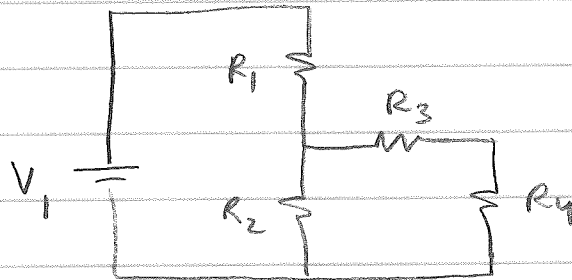

$$V_1 = 10 \text{ V}$$

$$R_1 = 12 \Omega$$

$$R_2 = 8 \Omega$$


$$R_3 = 5 \Omega$$

$$R_4 = 10 \Omega$$

a) Compute current through R_4 , first w/o using
Thevenin & Norton equivalents

Just treat as voltage divider. Want I_3

Kirchhoff's Rules

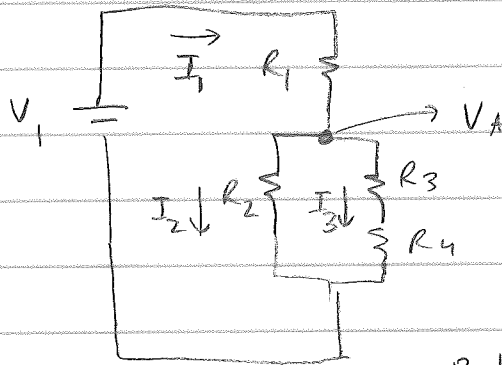

$$I_1 = I_2 + I_3$$

$$V_A = \frac{R_2 \parallel (R_3 + R_4)}{R_1 + R_2 \parallel (R_3 + R_4)} \cdot V_1$$

$$R_2 \parallel (R_3 + R_4) = \frac{R_2(R_3 + R_4)}{R_2 + (R_3 + R_4)}$$


$$= \frac{(8)(15)}{8 + 15} = 5.217 \Omega$$

$$V_A = (10 \text{ V}) \left(\frac{5.217}{12 + 5.217} \right) = 3.03 \text{ V}$$

$$I_3 = \frac{V_A}{R_3 + R_4} = \frac{3.03 \text{ V}}{(15 \Omega)} = \underline{\underline{0.202 \text{ A}}}$$

(6)

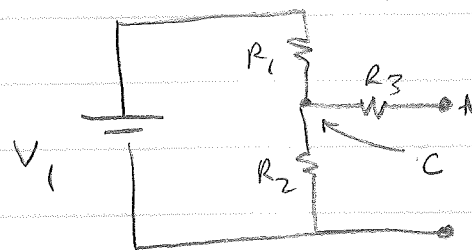b) $V_{Th} = V(\text{open})$ for circuit with R_4 removed




No current through R_3

$$\text{so } V_A = V$$


Use
voltage
divider

$$V_A = V_1 \frac{R_2}{R_1 + R_2} = (10) \left(\frac{8}{8 + 12} \right) = \underline{\underline{4V}}$$

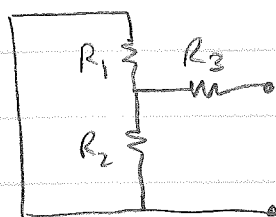R_{Th} is the equivalent resistance with V_1 shorted




same as
→

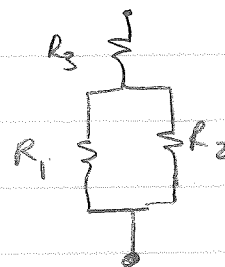

$$\begin{aligned} R_{eq} &= R_3 + R_1 \parallel R_2 \\ &= R_3 + \frac{R_1 R_2}{R_1 + R_2} \end{aligned}$$

$$R_{Th} = 5 + \frac{8 \cdot 12}{8 + 12} = \underline{\underline{9.8 \Omega}}$$

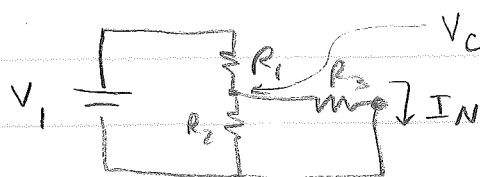Norton current: current with terminals shorted



V_C from voltage divider

$$V_C = V_1 \cdot \frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_1}$$


$$R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3}$$

$$V_C = (10V) \cdot \frac{\left(\frac{8 \cdot 5}{8 + 5} \right)}{\left(\frac{8 \cdot 5}{8 + 5} \right) + 12} = 2.04V$$

$$I_N = \frac{V_C}{R_3} = \frac{2.04}{5} = \underline{\underline{0.408A}}$$

- c) If $R_4 = 10 \Omega$ is connected across the Thevenin equivalent, we should get the answer from part a

Thevenin equivalent

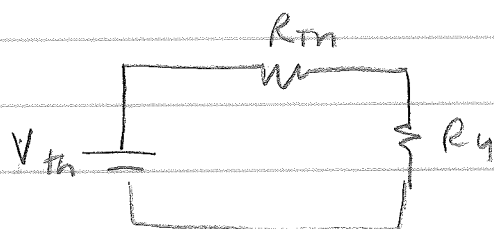


$$I_4 = \frac{V_{th}}{R_{th} + R_4} = \frac{4V}{(9.8 + 10)}$$

$$I_4 = \underline{\underline{0.202A}}$$

✓ same as part (a)

Norton equivalent

Thus
is a
current
divider

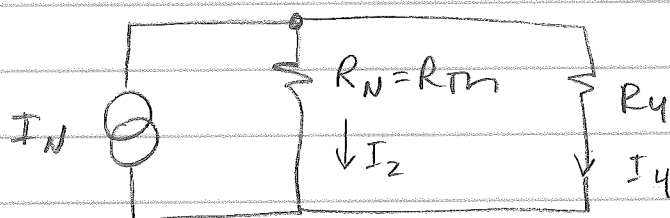

Both resistors
have the
same voltage
across them

$$I_4 = I_N - I_2 \quad I_4 R_4 = I_2 R_N$$

$$I_4 = I_N - \frac{I_4 R_4}{R_N}$$

$$I_4 \left(1 + \frac{R_4}{R_N}\right) = I_N$$

$$I_4 = I_N \left(\frac{R_N}{R_N + R_4} \right) = (0.408) \left(\frac{9.8}{9.8 + 10} \right) = \underline{\underline{0.202A}}$$

Again, same
answer, as expected