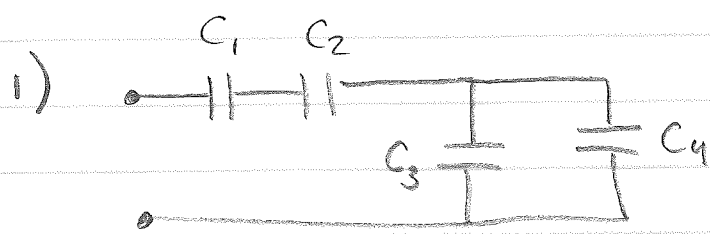


Homework #3 Solution



- $C_1 = 2.7 \mu F$
- $C_2 = 2.7 \mu F$
- $C_3 = 100 \mu F$
- $C_4 = 10 \mu F$

Capacitors in parallel: add

$$C_3 \parallel C_4 = C_3 + C_4$$

Capacitors in series: add reciprocals

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3 + C_4}$$

$$\frac{1}{C_{eq}} = \frac{C_1 + C_2}{C_1 C_2} + \frac{1}{C_3 + C_4} = \frac{(C_1 + C_2)(C_3 + C_4) + C_1 C_2}{C_1 C_2 (C_3 + C_4)}$$


$$\Rightarrow C_{eq} = \frac{C_1 C_2 (C_3 + C_4)}{(C_1 + C_2)(C_3 + C_4) + C_1 C_2}$$

$$= \frac{(2.7)(2.7)(110)}{(5.4)(110) + (2.7)(2.7)} \mu F$$

$$= \underline{\underline{1.33 \mu F}}$$

(2)

2)

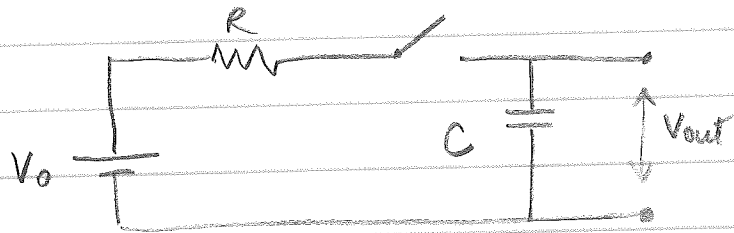

$$V_0 = 12V$$

$$R = 100k\Omega$$

$$C = 10\mu F$$

Want: V_{out} vs time after switch is closed

@ $t=0$ $Q=0$ on cap, $V_{out}=0$ @ $t=0$


RC circuit, charging capacitor

Time constant $\tau = RC = (100 \times 10^3)(10 \cdot 10^{-6}) = 1s$

Exponential

$$V_{out}(t) = V_0 (1 - e^{-t/RC})$$
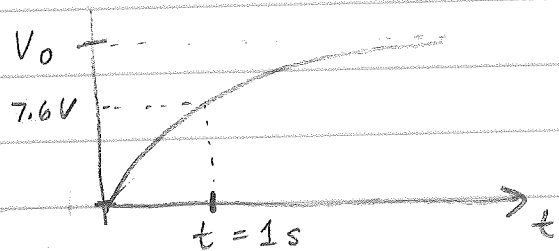
$$\begin{aligned} @ t=RC, V &= V_0(1 - 1/e) \\ &= V_0(0.63) = 7.6V \end{aligned}$$



3) $V_0 = 100V, R = 1M\Omega$

What is C for $V_{out} = 70V$ @ $t = 10.0s$?

$$V_{out} = V_0 (1 - e^{-t/RC})$$

$$1 - e^{-t/RC} = \frac{V_{out}}{V}$$

$$e^{-t/RC} = 1 - V_{out}/V$$

$$-t/RC = \ln(1 - V_{out}/V)$$

$$C = \frac{-t}{R \ln(1 - V_{out}/V)} = \frac{-10.0}{10^6 \ln(1 - 70/100)}$$

$$C = \underline{\underline{8.3 \mu F}}$$


4) Fully charge capacitor, then open switch

$$V_0 = 100 \text{ V}$$

$$C = 8.3 \mu\text{F}$$

$$R = 1 \text{ M}\Omega$$

$$V(t=0) = V_0$$

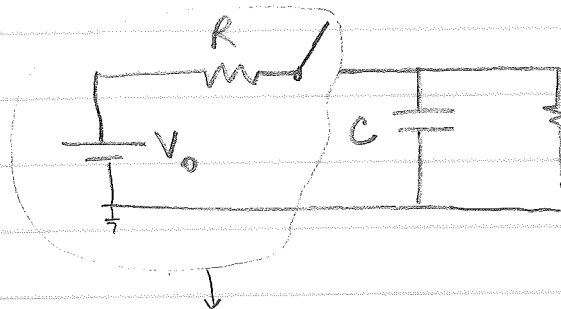

$$r = 10 \text{ k}\Omega$$

ignore this if switch opened

It's an RC discharge situation

$$V(t) = V_0 e^{-t/\tau C}$$

Solve for t s.t. $V = 1.0 \text{ V}$

$$e^{-t/\tau C} = \frac{V}{V_0}$$

$$-t/\tau C = \ln V/V_0$$

$$t = -\tau C \ln V/V_0 = (10 \times 10^3)(8.3 \mu\text{F}) \ln(0.01)$$

$$\underline{\underline{t = 0.38 \text{ s}}}$$

(4)

5) Sine wave , amplitude = 20 V_{pp}

$$R = 10\text{ k}\Omega$$

$$V(t) = (10\text{ V}) \sin(\omega t + \phi)$$

$$I(t) = \frac{V(t)}{R} = \left(\frac{10\text{ V}}{10^4\Omega} \right) \sin(\omega t + \phi)$$

$$I(t) = (1\text{ mA}) \sin(\omega t + \phi)$$

Peak current is 1 mA (or 2 mA_{pp})

Average current for a sine wave is 0

$$I_{rms} = \frac{1\text{ mA}}{\sqrt{2}} = \underline{\underline{0.707\text{ mA}}}$$

Power rating: use rms

$$P = I_{rms}^2 R$$

$$= (0.707 \times 10^{-3})^2 (10 \times 10^3)$$

$$P = \underline{\underline{5\text{ mW}}}$$

(or greater)