

Homework # 4 Solutions

RL circuit



Kirchoff's Loop Rule

$$-IR - L \frac{dI}{dt} = 0$$

$$\frac{dI}{dt} = - \frac{IR}{L}$$

$$\int_{I_0}^I \frac{dI}{I} = - \int_0^t \frac{R}{L} dt$$

$$\ln \frac{I}{I_0} = - \frac{R}{L} t$$

$$I = I_0 e^{-R/L t} = I_0 e^{-t/\tau}$$

$$\text{where } \tau = L/R$$

$$V(t) = I(t)R = I_0 R e^{-t/\tau}$$

Mechanical analogy:


$$Q \rightarrow x$$

$$I \rightarrow v$$

$$\rightarrow -vR - L \frac{dv}{dt} = 0 \quad \rightarrow \text{acceleration}$$


$$\text{like } \rightarrow ma = -bv \quad \text{in mechanics}$$

Like a constant drag force & velocity

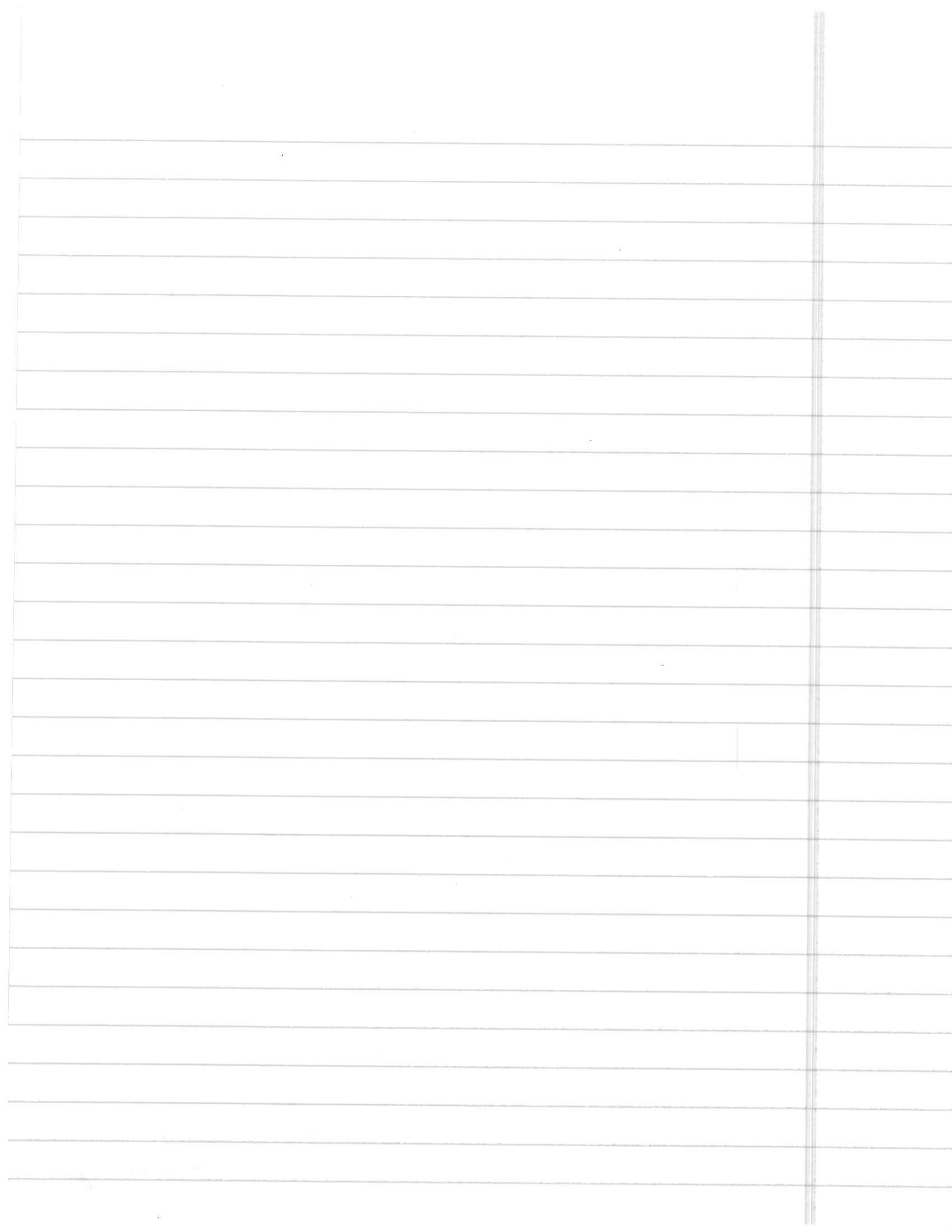

(2)

2.6)

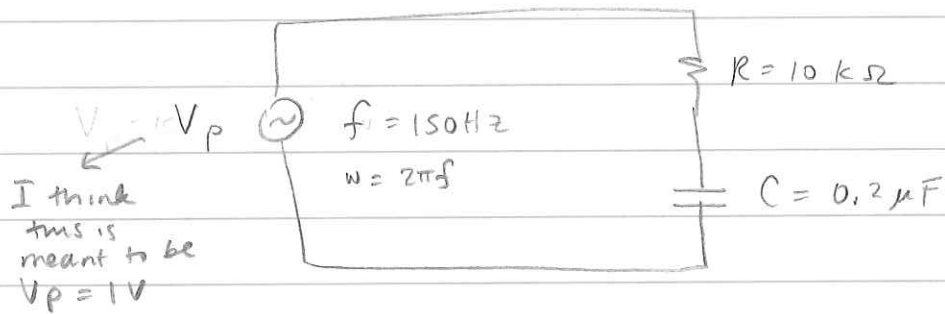

$$Z_{\text{tot}} = R + \frac{1}{j\omega C} = R - j\left(\frac{1}{\omega C}\right)$$

Magnitude $|Z| = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} = \sqrt{(10^3)^2 + \left(\frac{1}{(2\pi)(150)(0.2 \times 10^{-6})}\right)^2}$

$= \underline{\underline{11.3 \text{ k}\Omega}}$

Phase $\theta = \tan^{-1}\left(\frac{-1}{R\omega C}\right)$

$$= \tan^{-1}\left(\frac{-1}{(10 \times 10^3)(2\pi)(150)(0.2 \times 10^{-6})}\right)$$

$$= -0.488 \text{ rad}$$

$$= \underline{\underline{-27.95^\circ}}$$

$$2.7) \quad \omega = 10^3 \text{ rad/s}$$

$$\hat{V}_R = \hat{I} \hat{Z}_R$$

$$\hat{V}_C = \hat{I} \hat{Z}_C$$

$$\hat{I} = \frac{\hat{V}_P}{\hat{Z}_{tot}} = \frac{V_P e^{j\omega t}}{R - j/\omega C}$$

Across resistor:

$$\Rightarrow \hat{V}_R = \frac{V_P e^{j\omega t} R}{R - j/\omega C} = \frac{V_P R e^{j\omega t}}{R^2 + 1/\omega^2 C^2}$$

Across capacitor:

Peak amplitude is the magnitude

$$|\hat{V}_R| = \frac{V_P R}{R^2 + 1/\omega^2 C^2}^{1/2} = \frac{V_P R}{\sqrt{R^2 + 1/\omega^2 C^2}}$$

$$|\hat{V}_R| = \frac{(1 \text{ V})(10 \times 10^3)}{\left((10 \times 10^3)^2 + 1/((10^3)^2 (0.2 \times 10^{-6})^2) \right)^{1/2}}$$

$$|\hat{V}_R| = \underline{\underline{0.89 \text{ V}}}$$

Across capacitor: $\hat{V}_C = \frac{V_P e^{j\omega t} (1/j\omega C)}{R - j/\omega C} = \frac{V_P (-j/\omega C)(R + j/\omega C)}{(R^2 + 1/\omega^2 C^2)} e^{j\omega t}$

$$= V_P \left(\frac{1/\omega^2 C^2 - jR/\omega C}{(R^2 + 1/\omega^2 C^2)} \right) e^{j\omega t} = V_P \left(\frac{1 - jR\omega C}{1 + R^2 \omega^2 C^2} \right) e^{j\omega t}$$

$$|\hat{V}_C| = |V_P| \frac{(1 + R^2 \omega^2 C^2)^{1/2}}{(1 + R^2 \omega^2 C^2)^{1/2}} = |V_P| \frac{1}{(1 + R^2 \omega^2 C^2)^{1/2}}$$

$$= (1 \text{ V})$$


$$(1 + (10 \cdot 10^3)^2 (10^3)^2 (0.2 \times 10^{-6})^2)^{1/2}$$

$$|\hat{V}_C| = \underline{\underline{0.45 \text{ V}}}$$



(4)

2.8)

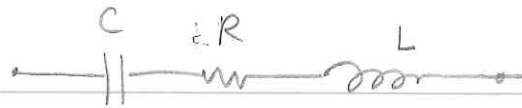

$$L = 1 \text{ H}$$

$$R = 1 \text{ k}\Omega$$

$$C = 2 \times 10^{-6} \text{ F}$$

$$\text{Resonant frequency } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{(2 \times 10^{-6})(1)}} = \underline{\underline{707 \text{ rad/s}}}$$

$$2.9) \quad \hat{Z} = R + j\omega L - \frac{1}{j\omega C}, \quad f = 2500 \text{ Hz}$$

$$\text{magnitude } |\hat{Z}| = \left(R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2 \right)^{1/2}$$

$$= \left(1000^2 + \left(2\pi(2500)(1) - \frac{1}{(2\pi)(2500)(2 \times 10^{-6})} \right)^2 \right)^{1/2}$$


$$|\hat{Z}| = \underline{\underline{15.7 \text{ k}\Omega}}$$

$$\text{Phase } \theta = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right) = \tan^{-1} \left(\frac{2\pi(2500)(1) - \frac{1}{(2\pi)(2500)(2 \times 10^{-6})}}{1000} \right)$$

+180/π

$$\theta = \underline{\underline{86.35^\circ}}$$

2.11)

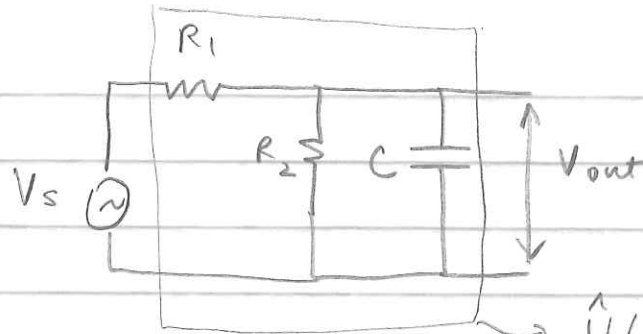

$$|V_{out}|/|V_{in}| = |\hat{H}(j\omega)| \quad \hat{H}(j\omega) \text{ describes network response}$$

Treat as
voltage
divider

$$\hat{H}(j\omega) = \frac{R_2 \parallel \hat{Z}_C}{R_2 \parallel \hat{Z}_C + R_1}$$

$$= \frac{R_2(-j/\omega C)}{R_2 - j/\omega C} = \frac{-(R_2/\omega C)j}{R_2(-j/\omega C) + R_1} = \frac{-(R_2/\omega C)j}{R_2 - j/\omega C + R_1}$$


$$= \frac{-R_2 j}{-jR_2 + R_1 R_2 \omega C - jR_1} = \frac{-R_2 j}{(R_1 R_2 \omega C) - j(R_2 + R_1)}$$

$$= \frac{-R_2 j (R_1 R_2 \omega C + j(R_1 + R_2))}{(R_1 R_2 \omega C)^2 + (R_1 + R_2)^2} = \frac{R_2(R_1 + R_2) - R_2 j R_1 R_2 \omega C}{(R_1 R_2 \omega C)^2 + (R_1 + R_2)^2}$$

$$|\hat{H}(j\omega)| = \frac{R_2}{(R_1 R_2 \omega C)^2 + (R_1 + R_2)^2} \left[(R_1 + R_2)^2 + (R_1 R_2 \omega C)^2 \right]^{1/2}$$

$$\boxed{\frac{|V_{out}|}{|V_{in}|} = |\hat{H}(j\omega)| = \frac{R_2}{\sqrt{(R_1 + R_2)^2 + (\omega C R_1 R_2)^2}}} \quad \text{as required}$$

2.12)

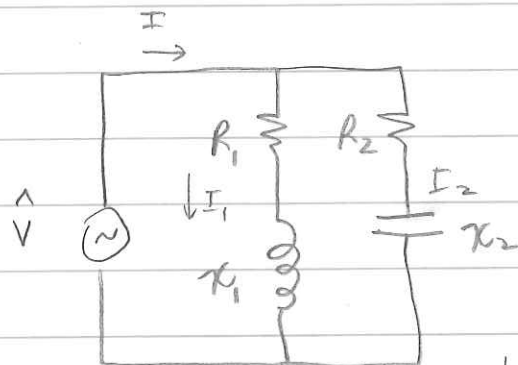

$$\hat{V} = \hat{Z}_{tot} \hat{I}$$

$$\hat{I} = \frac{\hat{V}}{\hat{Z}_{tot}}$$

$$\hat{Z}_{tot} = \frac{(R_1 + jX_1)(R_2 + jX_2)}{R_1 + jX_1 + R_2 + jX_2}$$

$$Z_{tot} = R_1 + jX_1 + R_2 + jX_2$$

Do this with Mathematica - see attached

$$[C_1, C_2, C_3, C_4, C_5, C_6, C_7, C_8, C_9, C_{10}, C_{11}, C_{12}, C_{99}, C_{100}]$$

$$[C_1, C_2, C_3, C_4, C_5, C_6, C_7, C_8, C_9, C_{10}, C_{11}, C_{12}, C_{99}, C_{100}]$$

I am having trouble with the Mathematica code

121

$$\hat{Z}_1 = jX_1 = j\omega L \quad (6)$$

$$\hat{Z}_2 = jX_2 = -53.1 \Omega$$

$$= -j/\omega C$$

$$-1/\omega C = X_2 = -53.1 \Omega$$

$$C = 1/(\omega X_2)$$

$$R_1 = 20 \Omega$$

$$X_1 = 37.7 \Omega \leftarrow \text{this means}$$

$$R_2 = 10 \Omega$$

$$X_2 = -53.1 \Omega$$

$$\hat{Z}_1 = j\omega L, \hat{Z}_2 = -j/\omega C$$

$$V_{rms} = 230 V$$

$$f = 60 \text{ Hz}, \omega = 2\pi(60) \frac{\text{rad}}{\text{s}}$$

$$V_{peak} = |\hat{V}| = \sqrt{2}(230) V$$

In[219]:= **ClearAll["Global`*"]**

In[220]:= **Z = (R1 + I chi1) * (R2 + I chi2) / (R1 + I chi1 + R2 + I chi2)**

Out[220]=
$$\frac{(i \text{ chi1} + R1) (i \text{ chi2} + R2)}{i \text{ chi1} + i \text{ chi2} + R1 + R2}$$

In[221]:= **Current = V / Z**

Out[221]=
$$\frac{(i \text{ chi1} + i \text{ chi2} + R1 + R2) V}{(i \text{ chi1} + R1) (i \text{ chi2} + R2)}$$

In[222]:= **omega = 2 Pi f**

Out[222]= $2 f \pi$

In[223]:= **Abs[Current]**

Out[223]=
$$\text{Abs} \left[\frac{(i \text{ chi1} + i \text{ chi2} + R1 + R2) V}{(i \text{ chi1} + R1) (i \text{ chi2} + R2)} \right]$$

In[224]:= **omega = 2 Pi f**

Out[224]= $2 f \pi$

In[225]:= **chi1 = 37.7**

Out[225]= 37.7

In[226]:= **chi2 = -53.1**

Out[226]= -53.1

In[227]:= **V = 230 (rms)**

Out[227]= 230

In[228]:= **Abs[Current] /. R1 -> 20 /. R2 -> 10 /. f -> 60.**

Out[228]= 3.36346
3.36 Arms $\rightarrow$ (note this is rms current)

In[229]:= **(Arg[Current] /. R1 -> 20 /. R2 -> 10 /. f -> 60.) * 180. / Pi**

Out[229]= -9.89206

-9.89° phase shift

