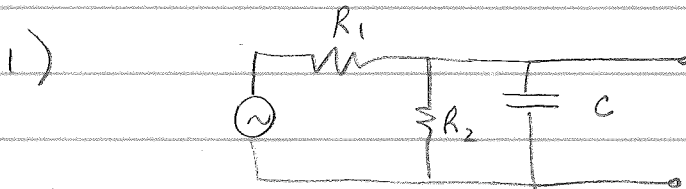


①

Homework #5 Solutions



$$\hat{H}(j\omega) = \frac{Z_{R_2 \parallel C}}{Z_{R_2 \parallel C} + R_1} = \frac{\frac{R_2 \cdot 1/j\omega C}{R_2 + 1/j\omega C}}{\frac{R_2 \cdot 1/j\omega C}{R_2 + 1/j\omega C} + R_1}$$

(same question as #10) which asks for $|H|$

$$= \frac{R_2 \cdot 1/j\omega C}{R_2 \cdot 1/j\omega C + R_1(R_2 + 1/j\omega C)}$$

$$= \frac{R_2}{R_2 + R_1 R_2 j\omega C + R_1}$$


$$\boxed{\hat{H}(j\omega) = \frac{R_2}{(R_1 + R_2) + j(R_1 R_2 \omega C)}} = \frac{R_2(R_1 + R_2) - j(R_1 R_2 \omega C)}{[(R_1 + R_2)^2 + (R_1 R_2 \omega C)^2]}$$

We are not given numerical values, so plot in terms of corner frequency

"Regime change" when $(R_1 + R_2) = R_1 R_2 \omega C$
for $\omega = \omega_c = \frac{(R_1 + R_2)}{R_1 R_2 C}$

Sketch: $\omega \gg \omega_c$, $|H| \propto \omega^{-1}$
 $\omega \ll \omega_c$, $|H| \sim R_2/(R_1 + R_2)$ | low-pass


2

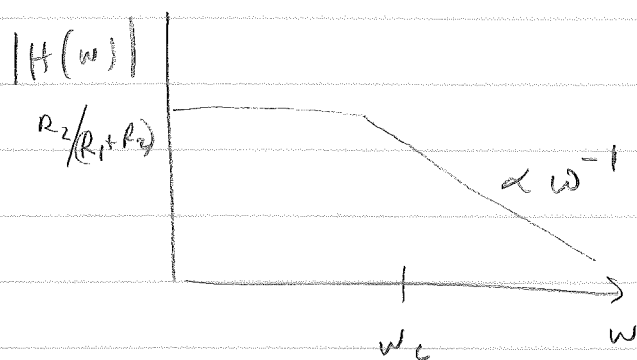

$$\begin{aligned}
 |H| &= \frac{R_2}{((R_1 + R_2)^2 + (w R_1 R_2 C)^2)^{1/2}} = \frac{R_2}{(R_1 + R_2) \left[1 + \left(\frac{R_1 R_2 C}{R_1 + R_2} w \right)^2 \right]^{1/2}} \\
 &= \frac{R_2}{(R_1 + R_2) \left[1 + \left(\frac{w}{w_c} \right)^2 \right]^{1/2}}
 \end{aligned}$$

Phase shift $H(jw) = \frac{R_2[(R_1 + R_2) - (R_1 R_2 w C)j]}{(R_1 + R_2)^2 + (R_1 R_2 w C)^2}$
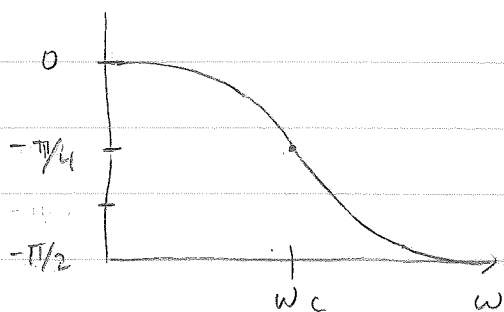
$$\theta = \tan^{-1} \left(\frac{-R_1 R_2 w C}{R_1 + R_2} \right) = \tan^{-1} \left(-\frac{w}{w_c} \right)$$



Low-pass filter type phase shift

(3)

2) To show: $P_{avg} = \frac{1}{2} \text{Re}(\hat{V}^* \hat{I}) = \frac{1}{2} \text{Re}(\hat{V} \hat{I}^*)$

Write these as $\hat{V} = V_0 e^{j(\omega t + \phi_1)}$
 $\hat{I} = I_0 e^{j(\omega t + \phi_2)}$

$P(t) = \underbrace{V(t) I(t)}_{\text{real parts}} = V_0 \cos(\omega t + \phi_1) I_0 \cos(\omega t + \phi_2)$

$P_{avg} = \frac{1}{T} \int_0^T V(t) I(t) dt$ over one cycle

$= \frac{V_0 I_0}{T} \int_0^T \cos(\omega t + \phi_1) \cos(\omega t + \phi_2) dt$

$\cos(A+B) = \cos A \cos B - \sin A \sin B$

$= \frac{V_0 I_0}{T} \int_0^T [\cos \omega t \cos \phi_1 - \sin \omega t \sin \phi_1] [\cos \omega t \cos \phi_2 - \sin \omega t \sin \phi_2] dt$

odd functions integrated over a cycle
(with single $\sin \omega t$) are zero

$= \frac{V_0 I_0}{T} \int_0^T [\cos^2 \omega t \cos \phi_1 \cos \phi_2 + \sin^2 \omega t \sin \phi_1 \sin \phi_2] dt$

$\cos(\phi_1 - \phi_2)$

$= \cos \phi_1 \cos \phi_2 + \sin \phi_1 \sin \phi_2$

$= \frac{V_0 I_0}{T} \left[\underbrace{\int_0^T [\cos^2 \omega t] dt}_{T/2} \cos \phi_1 \cos \phi_2 + \underbrace{\int_0^T [\sin^2 \omega t] dt}_{T/2} \sin \phi_1 \sin \phi_2 \right]$

$= \frac{V_0 I_0}{2} [\underbrace{\cos \phi_1 \cos \phi_2 + \sin \phi_1 \sin \phi_2}_{\cos(\phi_1 - \phi_2)}]$

$\Rightarrow P_{avg} = \frac{V_0 I_0}{2} \cos(\phi_1 - \phi_2)$


(4)

$$\begin{aligned}
\frac{1}{2} \operatorname{Re}(\hat{V}^* \hat{I}) &= \frac{1}{2} \operatorname{Re} \left[V_0 e^{-j(\omega t + \phi_1)} I_0 e^{j(\omega t + \phi_2)} \right] \\
&= \frac{V_0 I_0}{2} \operatorname{Re} \left[e^{j(\phi_1 + \phi_2)} \right] \\
&= \frac{V_0 I_0}{2} \cos(-\phi_1 + \phi_2) \\
&= \frac{V_0 I}{2} \cos(\phi_1 - \phi_2) \quad , \text{ same result}
\end{aligned}$$

$$\begin{aligned}
\frac{1}{2} \operatorname{Re}(\hat{V} \hat{I}^*) &= \frac{1}{2} \operatorname{Re} \left[V_0 e^{j(\omega t + \phi_1)} I_0 e^{-j(\omega t + \phi_2)} \right] \\
&= \frac{V_0 I_0}{2} \operatorname{Re} \left[e^{j(\phi_1 - \phi_2)} \right] \\
&= \frac{V_0 I_0}{2} \cos(\phi_1 - \phi_2) \quad , \text{ again same result}
\end{aligned}$$

(5)

2.10) RC low-pass filter with $\frac{|V_{out}|}{|V_{in}|} = 0.5 @ f = 5 \text{ kHz}$

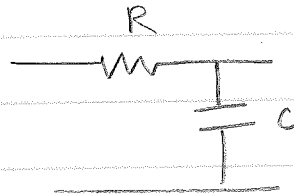

$$H = \frac{1}{1 + j\omega RC} = \frac{1 - j\omega RC}{1 + \omega^2 (RC)^2}$$

$$\frac{|V_{out}|}{|V_{in}|} = |H| = \frac{1}{(1 + \omega^2 (RC)^2)^{1/2}} = \frac{1}{(1 + (\omega/\omega_c)^2)^{1/2}}$$

$$\text{for } \frac{|V_{out}|}{|V_{in}|} = 0.5 = \frac{1}{(1 + (\omega/\omega_c)^2)^{1/2}}$$

$$1 + \frac{\omega^2}{\omega_c^2} = \frac{1}{0.5^2}$$

$$\frac{\omega^2}{\omega_c^2} = \frac{1}{0.5^2} - 1$$

$$\omega_c^2 = \frac{\omega^2}{\frac{1}{0.5^2} - 1}$$


$$\omega = 2\pi f = 2\pi(5 \times 10^3)$$

$$\Rightarrow \omega_c = 18.1 \text{ rad/s} = 28.5 \text{ kHz}$$

$$\left. \begin{aligned} RC &= \frac{1}{\omega_c} \\ &= 5.5 \times 10^{-5} \text{ s}^{-1} \end{aligned} \right\} \text{so choose, say } \begin{aligned} R &= 1 \text{ k}\Omega \\ C &= \frac{1}{\omega_c R} = \underline{5.5 \times 10^{-8} \text{ F}} \end{aligned}$$

(any combination with specified product OK)

(6)

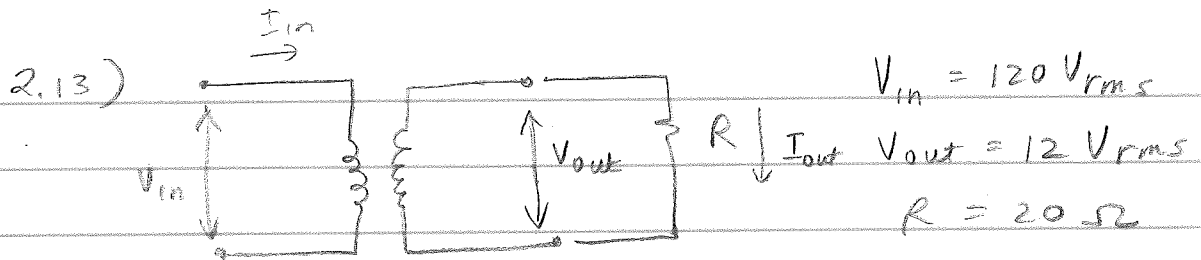

$$V_{out} = \left(\frac{n_2}{n_1} \right) V_{in}$$

$$\text{Turns ratio} = \frac{n_2}{n_1} = \frac{V_{out}}{V_{in}} = \frac{12}{120} = 0.1$$


In Secondary $I_{out} = \frac{V_{out}}{R} = \frac{12 V_{rms}}{20 \Omega} = 0.6 A_{rms}$

In primary $I_{in} = \left(\frac{n_2}{n_1} \right) I_{out} = (0.1)(0.6 A_{rms})$

$$I_{in} = \underline{\underline{0.06 A_{rms}}}$$

2.14) Audio signal generator

$$Z_{out} = 600 \Omega$$

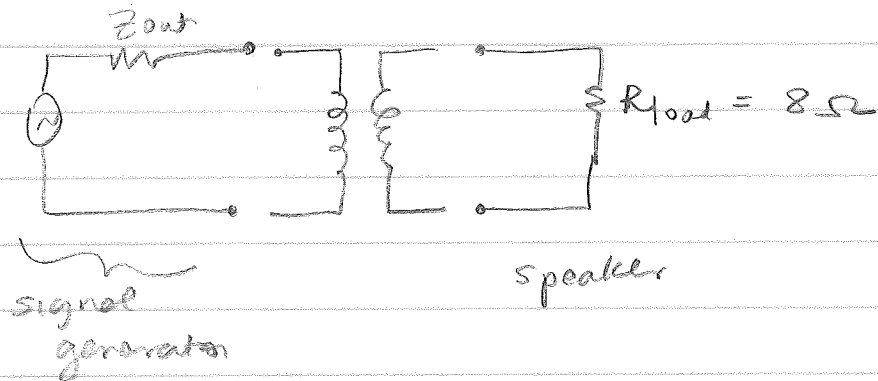

Impedance matching $R_{eff} = \left(\frac{n_1}{n_2} \right)^2 R_L$, want $R_{eff} = 600 \Omega$

$$\text{Want } \left(\frac{n_1}{n_2} \right) = \sqrt{\frac{R_{eff}}{R_L}} = \sqrt{\frac{600}{8}} = 8.66$$

2.15) Step-down transformer has 1.6Ω

Impedance on one side, 40Ω on the other

$$\left. \begin{aligned} Z_2 &= \frac{V_2}{I_2} = \frac{(n_2/n_1)V_1}{(n_1/n_2)I_1} \\ Z_2 &= \left(\frac{n_2}{n_1}\right)^2 Z_1 \end{aligned} \right\} \Rightarrow \frac{n_1}{n_2} = \sqrt{\frac{Z_1}{Z_2}} = \sqrt{\frac{1.6}{40}} = 0.2$$

It's a step-down transformer

so primary side has larger n



$\Rightarrow$ side 2 is the primary
side 1 is the secondary


$$V_{out} = \left(\frac{n_2}{n_1}\right) V_{in}$$

$$\Rightarrow V_{out} = 0.2 (120 V_{rms}) = \underline{\underline{24 V_{rms}}}$$

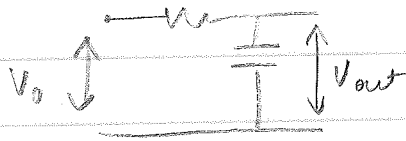2.16) Low pass filter $\omega_c = 2\pi(100 \text{ Hz})$

Square wave
amplitude V_0

$$\omega = 2\pi f = (2\pi)90 \text{ Hz}$$



$$|H| = \frac{1}{(1 + (\omega/\omega_c)^2)^{1/2}}$$

$$\frac{\omega}{\omega_c} = \frac{90}{100} = 0.9$$

Attenuates
frequencies
greater than
 $\sim \omega_c$

As per example in class, a square wave consists of a sum of sinusoids (see handout)

$\omega, 3\omega, 5\omega, \dots$; coefficients $V_0\left(\frac{2}{\pi}, -\frac{2}{3\pi}, \frac{2}{5\pi}, \dots\right)$

$$f(t) = a_0 + \left(\frac{2}{\pi}\right)V_0 \cos \omega_1 t - \left(\frac{2}{3\pi}\right)V_0 \cos \omega_3 t + \dots$$

The filter attenuates all components with $\omega > 2\pi(100 \text{ Hz})$,
so the only remaining component
of the square wave will be the
fundamental, $\omega = 2\pi(90 \text{ Hz})$

The output will look like a ^(slightly) distorted


90 Hz sinusoid, amplitude $\frac{2V_0}{\pi}$ (first term of Fourier series from class)

Amplitude out:

$$V_{out} \sim \frac{1}{(1 + (\omega/\omega_c)^2)^{1/2}} \cdot \frac{2V_0}{\pi}$$

$$= \frac{1}{(1 + (0.9)^2)^{1/2}} \cdot \frac{2}{\pi} (V_0)$$
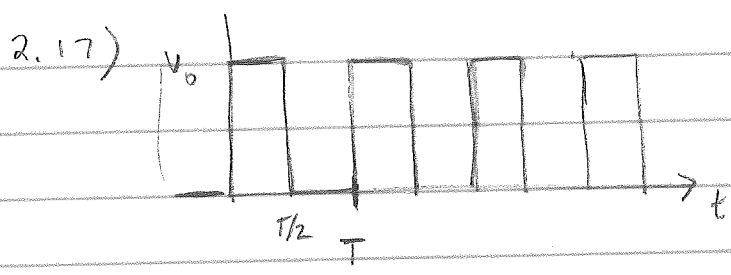
$$\sim \underline{\underline{0.47 V_0}}$$



$$f(t) = V_0 \quad 0 \leq t < T/2$$
$$= 0, \quad T/2 \leq t < T$$

This is the square wave from class with $\frac{V_0}{2}$ offset (see handout) and a phase shift

$$f(t) = a_0 + 2 \sum_{n=1}^{\infty} (a_n \cos(n\omega_1 t) - b_n \sin(n\omega_1 t))$$

$$\omega = \frac{2\pi}{T}$$

In this case, the function is odd, so we can drop the a_n terms, keep the b_n ones

$$n=0 \quad a_0 = \frac{1}{T} \int_{\text{one cycle}} f(t) \cos(0) dt = \frac{1}{T} \int_0^{T/2} V_0 dt = \frac{V_0}{2}$$

$$n=1,2,\dots \quad b_n = -\frac{1}{T} \int_0^{T/2} V_0 \sin(n\omega_1 t) dt = -\frac{V_0}{T} \left[\frac{-\cos(n\omega_1 t)}{n\omega_1} \right]_0^{T/2}$$
$$\omega_1 = 2\pi/T$$

$$= \frac{V_0}{n \cdot 2\pi} \left[\cos\left(\frac{n\omega_1 T}{2}\right) - 1 \right] = \frac{V_0}{2\pi n} \left[\cos(n\pi) - 1 \right]$$

$$b_m = -\frac{2V_0}{(2\pi)(2m-1)} \quad m=1,2,\dots$$
$$\left. \begin{array}{l} n=1 \rightarrow -2 \\ n=2 \rightarrow 0 \\ n=3 \rightarrow -2 \end{array} \right\} \begin{array}{l} \text{only} \\ \text{odd} \\ \text{ } n\text{'s} \\ \text{left} \end{array}$$

$$f(t) = \frac{V_0}{2} - \frac{2V_0}{2\pi} \left[-2 \sin(\omega_1 t) - \frac{2 \sin(3\omega_1 t)}{3} - \frac{2 \sin(5\omega_1 t)}{5} - \dots \right]$$

$$f(t) = \frac{V_0}{2} + \frac{2V_0}{\pi} \left[\sin \omega_1 t + \frac{1}{3} \sin 3\omega_1 t + \frac{1}{5} \sin 5\omega_1 t + \dots \right]$$