

①

Homework # 6 Solutions

Problem 1 Fourier Theorem

Periodic function w/ period T

$$f(t) = \sum_{n=-\infty}^{\infty} \hat{C}_n e^{j\omega_n t}, \quad \hat{C}_n = \frac{1}{T} \int_{t'}^{t'+T} f(t) e^{-j\omega_n t} dt$$

$$\omega_n = \frac{2\pi n}{T} = n\omega_1$$

$$f(t) = \sum_{n=-\infty}^{\infty} \hat{C}_n [\cos \omega_n t + j \sin \omega_n t] \quad \omega_1 = \frac{2\pi}{T}$$

$$= \hat{C}_0 [\cos(0) + j \sin(0)] + \sum_{n=-\infty}^{-1} \hat{C}_n [\cos(n\omega_1 t) + j \sin(n\omega_1 t)] + \sum_{n=1}^{\infty} \hat{C}_n [\cos(n\omega_1 t) + j \sin(n\omega_1 t)]$$

$\nwarrow$ even $\nwarrow$ odd for $n \rightarrow -n$

$$= \hat{C}_0 + \sum_{n=1}^{\infty} \hat{C}_n \cos(n\omega_1 t) + \sum_{n=-\infty}^{-1} \hat{C}_n \cos(n\omega_1 t) + j \left[\sum_{n=1}^{\infty} \hat{C}_n \sin(n\omega_1 t) + \sum_{n=-\infty}^{-1} \hat{C}_n \sin(n\omega_1 t) \right]$$

We have

$$\hat{C}_n = \frac{1}{T} \int_{t'}^{t'+T} f(t) [\cos(n\omega_1 t) - j \sin(n\omega_1 t)] dt$$

$$\Rightarrow \hat{C}_n = a_n + j b_n$$

$$\hat{C}_{-n} = \frac{1}{T} \int_{t'}^{t'+T} f(t) [\cos(n\omega_1 t) + j \sin(n\omega_1 t)] dt$$

$$\Rightarrow \hat{C}_{-n} = a_n - j b_n$$

Now plug in

(2)


$$f(t) = \hat{C}_0 + \sum_{n=1}^{\infty} \hat{C}_n \cos(n\omega_1 t) + \sum_{n=1}^{\infty} \hat{C}_{-n} \cos(n\omega_1 t) \\ + j \sum_{n=1}^{\infty} \hat{C}_n \sin(n\omega_1 t) - j \sum_{n=1}^{\infty} \hat{C}_{-n} \sin(n\omega_1 t)$$

$$f(t) = \hat{C}_0 + \sum_{n=1}^{\infty} \left[(a_n + j b_n) \cos(n\omega_1 t) + (a_n - j b_n) \cos(n\omega_1 t) \right. \\ \left. + j (a_n + j b_n) \sin(n\omega_1 t) - j (a_n - j b_n) \sin(n\omega_1 t) \right]$$

$$\boxed{f(t) = \hat{C}_0 + 2 \sum_{n=1}^{\infty} [a_n \cos(n\omega_1 t) - b_n \sin(n\omega_1 t)]}$$

which is in the required form

(3)

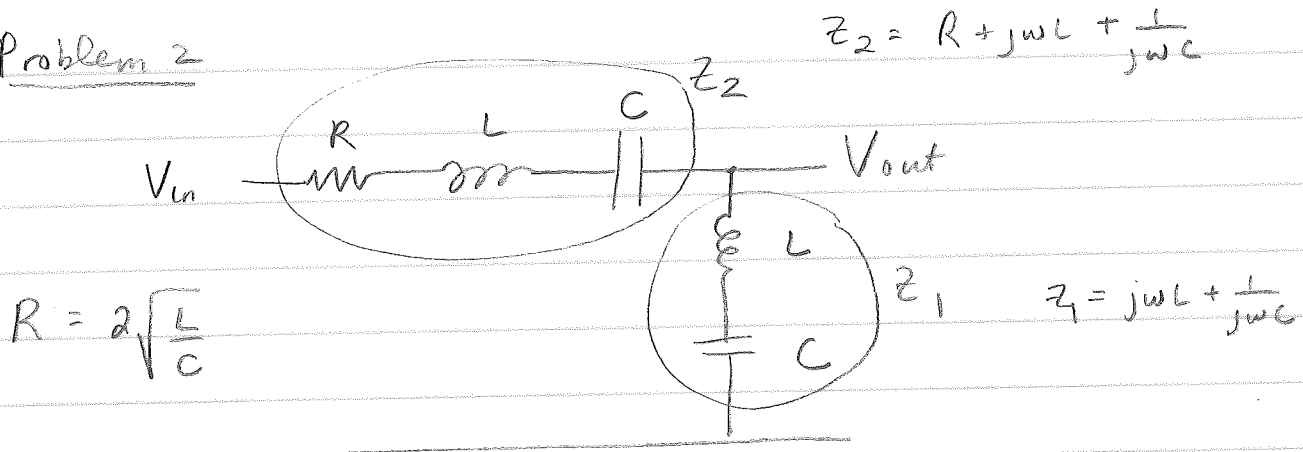Problem 2

Treat as voltage divider

Transfer function $H(j\omega) = \frac{Z_1}{Z_1 + Z_2}$

$$H(j\omega) = \frac{j\omega L + \frac{1}{j\omega C}}{R + 2(j\omega L) + \frac{2}{j\omega C}} \quad j\omega \rightarrow s$$

$$\hat{H}(\hat{s}) = \frac{\hat{s}L + \frac{1}{\hat{s}C}}{R + 2\hat{s}L + \frac{2}{\hat{s}C}} = \frac{\hat{s}^2 LC + 1}{\hat{s}RC + 2\hat{s}^2 LC + 2}$$

Plug in $R = 2\sqrt{L/C}$ $\hat{H}(\hat{s}) = \frac{\hat{s}^2 LC + 1}{2\hat{s}\sqrt{LC} + 2\hat{s}^2 LC + 2}$

$$H(s) = \frac{\hat{s}^2 LC + 1}{2(1 + \sqrt{LC}\hat{s} + LC\hat{s}^2)}$$

Zeros: $\hat{s}^2 LC + 1 = 0$


$$\hat{s} = \pm j\sqrt{\frac{1}{LC}}$$

Poles: $1 + \hat{s}\sqrt{LC} + LC\hat{s}^2 = 0$

$$\begin{aligned} a &= LC \\ b &= \sqrt{LC} \\ c &= 1 \end{aligned}$$

$$\hat{s} = \frac{-\sqrt{LC} \pm \sqrt{LC - 4LC}}{2LC} = \frac{-1}{2\sqrt{LC}} \pm j\frac{\sqrt{3}}{2\sqrt{LC}}$$

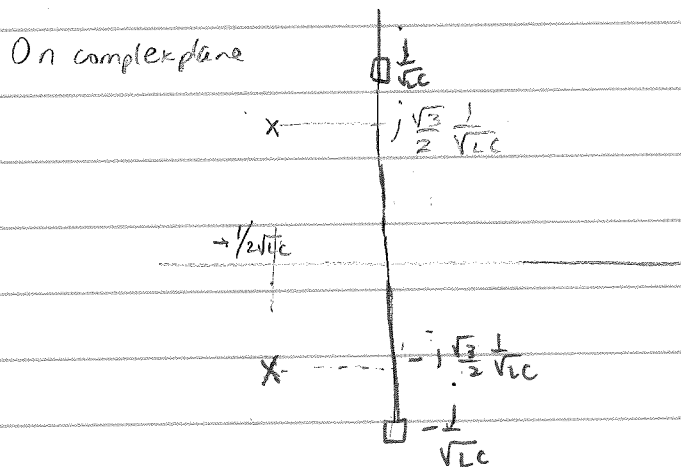Poles: $s_{\pm} = \frac{1}{2\sqrt{LC}} (-1 \pm j\sqrt{3})$



Bode plot

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$s^2 \rightarrow -\omega^2$$


$$s \rightarrow j\omega$$

Write as $\hat{H}(j\omega) = \frac{-\omega^2/\omega_0^2 + 1}{2(1 + j\omega/\omega_0 - \omega^2/\omega_0^2)}$

$$\omega \rightarrow \infty \quad |\hat{H}| \propto 1/2$$

$$\omega \rightarrow 0 \quad |\hat{H}| \propto -1/2$$

zero for $\omega = \omega_0$

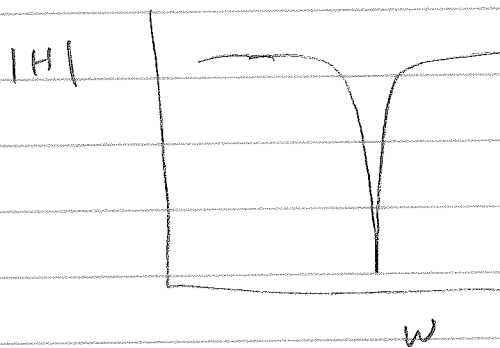

A notch filter

5


```
In[58]:= ClearAll["Global`*"]
```

```
In[59]:= H = (1 - omega^2 / omega0^2) / (2 (1 + I omega / omega0 - omega^2 / omega0^2))
```

```
Out[59]= 
$$\frac{1 - \frac{\omega^2}{\omega_0^2}}{2 \left( 1 - \frac{\omega^2}{\omega_0^2} + \frac{i \omega}{\omega_0} \right)}$$

```
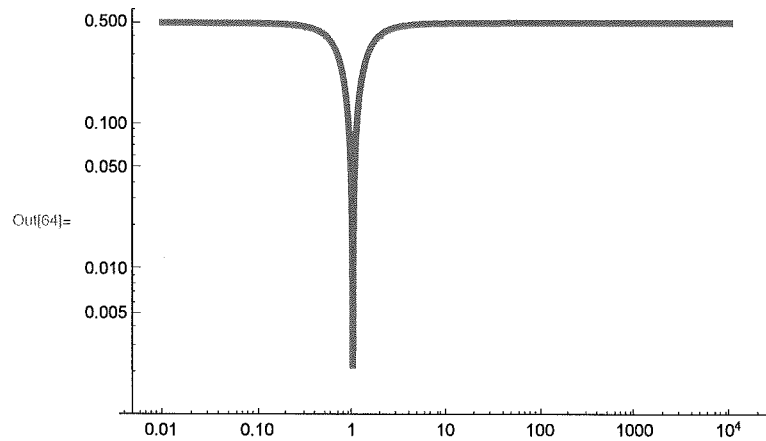
```
In[64]:= LogLogPlot[Abs[H] /. omega0 -> 1, {omega, 0.01, 10000.},  
PlotStyle -> Thickness[0.01], PlotRange -> {0.001, 0.6}]
```




2.18) Sawtooth signal, $T_{\text{saw}} = 1 \text{ ms}$, V_p at peak
 $V_p = 1 \text{ V}$

Want a circuit that will give a 3 kHz sinusoid as output

Want

$$T = \frac{1}{f} = \frac{1}{3 \times 10^3}$$

$$T = \frac{1}{3} \text{ ms}$$

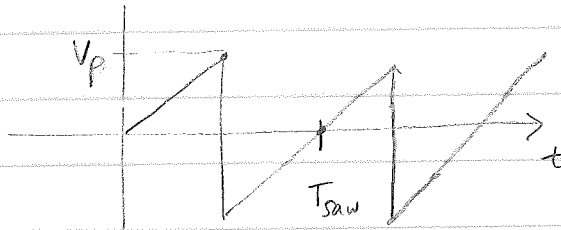


$$\omega_{\text{saw}} = \frac{2\pi}{T_{\text{saw}}}$$

We saw the Fourier components of the sawtooth in Section 2.8

$$f(t) = \frac{2V_p}{\pi} \left[\sin[\omega_{\text{saw}} t] - \frac{1}{2} \sin(2\omega_{\text{saw}} t) + \frac{1}{3} \sin(3\omega_{\text{saw}} t) - \frac{1}{4} \sin(4\omega_{\text{saw}} t) + \dots \right]$$

we want this component only
 which has $3 \times$ the frequency

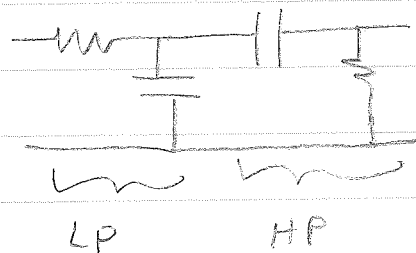$\Rightarrow$ design a bandpass filter that removes frequencies higher and lower than $\omega = 2\pi/3 \times 10^3$ rad/s
 $= 18.8 \text{ rad/s} \times 10^2$



2nd stage should have higher impedance (or else buffer)

Higher impedance $\downarrow$

choose $\omega_{C_{LP}} = 4\omega_{\text{saw}}$

$$R = 100 \Omega$$

$$C = \frac{1}{4(100)(18.8 \times 10^2)} = 1.3 \times 10^{-7} \text{ F}$$

$\omega_{C_{HP}} = 2\omega_{\text{saw}}$

$$R = 10 \text{ k}\Omega$$

$$C = \frac{1}{2(10^4)(18.8 \times 10^2)} = 2.6 \times 10^{-9} \text{ F}$$

$$\omega = \frac{1}{RC}$$


$$C = \frac{1}{R\omega}$$

(7)

But a more efficient way is with a bandpass LRC circuit, like the one in class.

$$\omega_1 = \frac{1}{RC}$$

$$\omega_2 = \frac{R}{L}$$

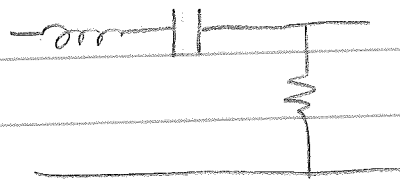

$$\hat{H} = \frac{j\omega/\omega_1}{(1 - \omega^2/\omega_1\omega_2 + j\omega/\omega_1)}$$

$$\text{Choose } \sqrt{\omega_1\omega_2} = \omega_0 = \frac{1}{\sqrt{LC}} = 2\pi(3 \text{ kHz})$$

(resonant frequency)

$$\text{Choose } LC = (2\pi 3 \times 10^3)^{-2} = 2.8 \times 10^{-9}$$

$$\text{Choose } C = 10^{-6} \text{ F}, L = 2.8 \text{ mH}$$

We want reasonable attenuation of $2\omega_{\text{saw}}$ and $4\omega_{\text{saw}}$, so need to choose a relatively small R

$$R = 5 \Omega \quad (\text{check with plot - looks fine})$$

Amplitude of filtered sine wave will be

$$\sim \frac{2V_p}{\pi} \left(\frac{1}{3} \right) = \frac{2(1)}{\pi 3} = \underline{\underline{0.212 \text{ V}}}$$

In[157]:= **ClearAll["Global`*"]**

In[158]:= **Hbp = I (omega / omega1) / (1 - omega^2 / (omega1 omega2)) + I omega / omega1**

Out[158]=
$$\frac{i \omega}{\omega_1} + \frac{i \omega}{\omega_1 \left(1 - \frac{\omega^2}{\omega_1 \omega_2}\right)}$$

In[159]:= **omega1 = 1 / (R Cap)**

Out[159]=
$$\frac{1\,000\,000}{R}$$

In[160]:= **omega2 = R / L**

Out[160]=
$$\frac{R}{L}$$

In[161]:= **R = 5; L = 2.8 × 10⁻³; Cap = 10⁻⁶;**

In[167]:= **1 / Sqrt[L Cap]**

Out[167]= 18 898.2


In[162]:= **Abs[Hbp] /. omega → 2 Pi 3000.**

Out[162]= 18.4166

In[163]:= **wsaw = 2 Pi 1000.**


Out[163]= 6283.19

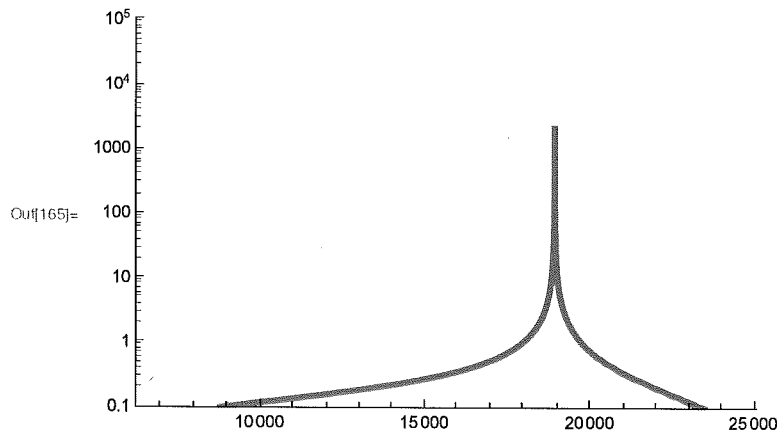In[165]:= **LogPlot[Abs[Hbp], {omega, wsaw, 4 wsaw},
PlotStyle → Thickness[0.01], PlotRange → {{wsaw, 4 wsaw}, {0.1, 100 000.}}]**



3.1) These are basically in the text
p-n junction


No bias

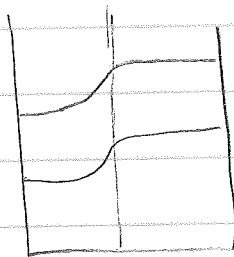

n (+) p (-)

Net current is zero

Reverse bias

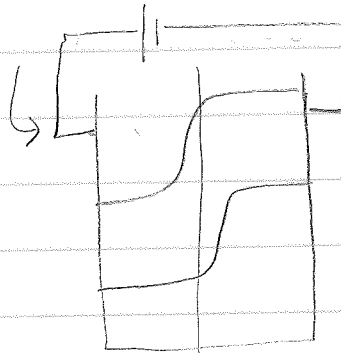


n (+) p (-)
more more

→
Small current
from n to p



Forward bias

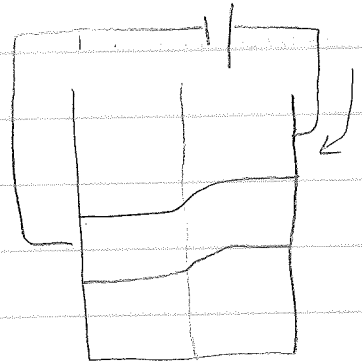

n (+) p (-)

←
larger current
from p to n

