

Homework 7 Solutions


3.2)

a)


Use simplified diode model

$$f = 100 \text{ Hz}$$


$$V_p = 5 \text{ V}$$

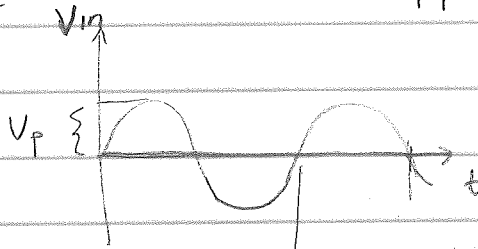

$$T = 0.01 \text{ s}$$

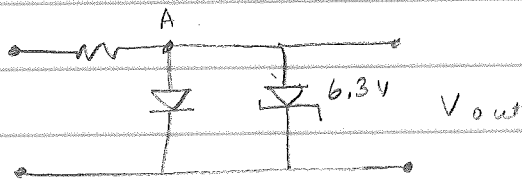

Clipper circuit

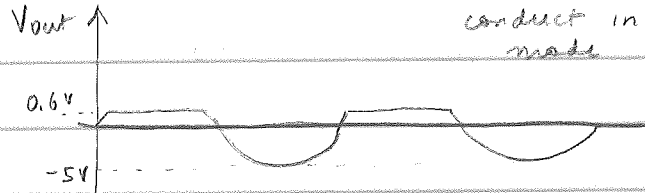


If $V_A = V_{out} > 0.6 \text{ V}$
the normal diode conducts, $V_A = V_{pn} = 0.6 \text{ V}$



The Zener does not conduct in breakdown mode

For $V_A < 0.6 \text{ V}$,
output follows input

same period T

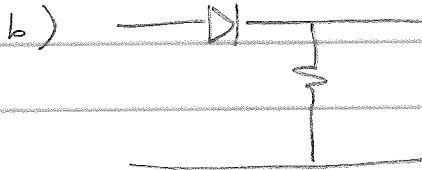

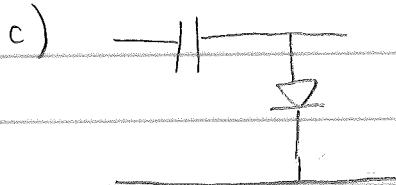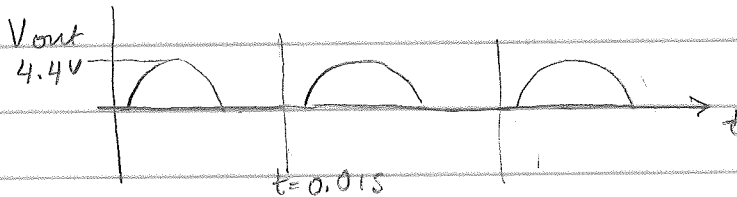
This is a half-wave rectifier,
diode conducts and
 $V_{out} = V_{in} - 0.6 \text{ V}$ for $V_{out} > 0.6 \text{ V}$




This is a clamper.

Output is shifted down
by $V_p - 0.6 \text{ V} = 4.4 \text{ V}$

(assume capacitor has a large
value)

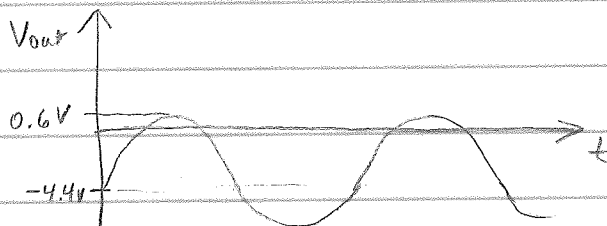


same period T

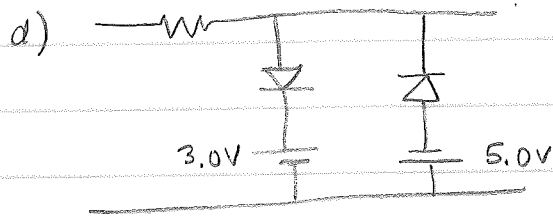


Another clipper,
except output cannot
be more positive than
 $3.0\text{V} + 0.6\text{V}$

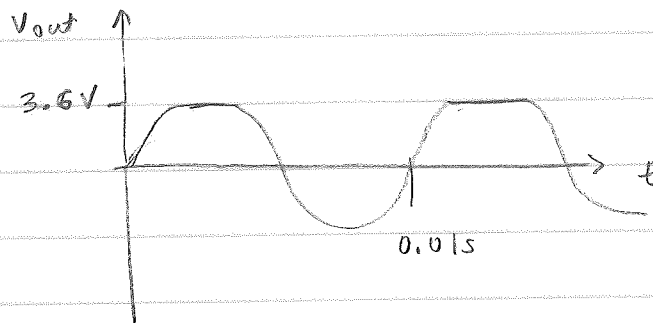or more negative than
 $-5.0 - 0.6\text{V}$




↳ this signal always has
 $> -5\text{V}$, so never gets
negatively clipped

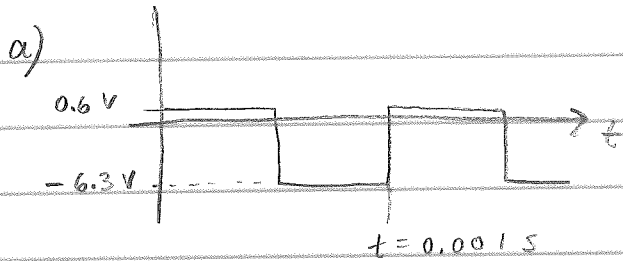3.3) Same explanations as for problem 3.2 apply, except that input $V_p = 10\text{ V}$, and output period follows the input with $T = 0.001\text{ s}$ period (and it's a square wave)




clippers

Here the zener limits the negative swing

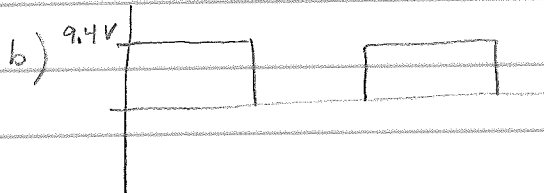


Conducts only on positive side

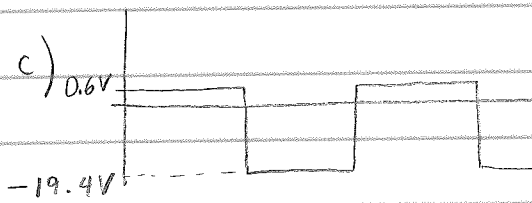


clamp shifts down by

$$V_p - 0.6 = 9.4\text{ V}$$

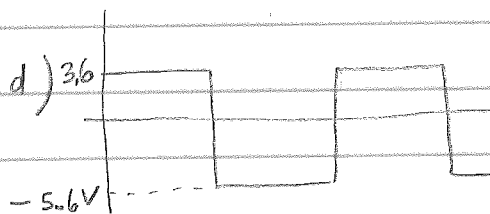

clamp, limits to +3.6 V, -5.6 V

(4)

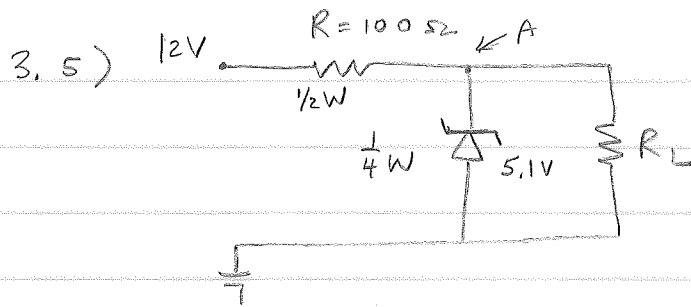

a) What happens if R_L is shorted?

$$V_A = 0, \text{ all}$$

$$\text{Power through } R \text{ is } P = \frac{V^2}{R} = \frac{12^2}{100} = 1.44 \text{ W}$$

The resistor is only rated for 0.5 W
so sadly, it burns out

b) What happens if R_L is removed?

All the current must flow through the Zener

$$V_A = 5.1 \text{ V}$$


$$I = \frac{12 \text{ V} - V_A}{R} = 0.069 \text{ A}$$

$$P_R = I^2 R = (0.069)^2 (100) = 0.48 \text{ W} \text{ resistor survives}$$

$$P_Z = IV = (0.069)(5.6) = 0.35 \text{ W}$$

which exceeds the Zener power rating
So bad news for the Zener.

3.6) Zener diode voltage regulator

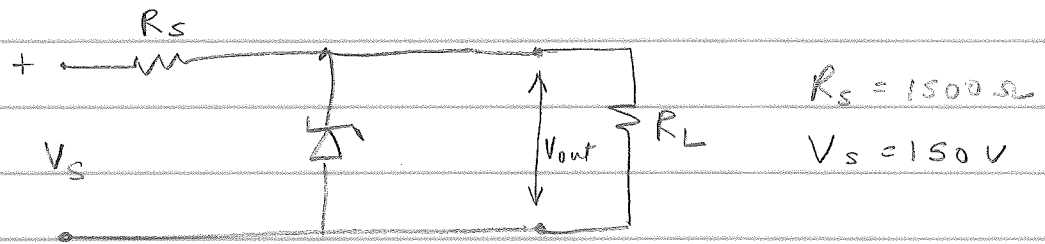

a) Want: range of R_L over which $V_{out} = \text{constant}$

Zener breaks down @ $100 V = V_Z$

I_{max} through Zener = 100 mA

Want the Zener in breakdown mode, in which case

we have $V_{out} = 100 V$

Breakpoint at $V_{out} = V_s \frac{R_L}{R_L + R_s}$ (voltage divider)

$$V_{out} = \frac{V_s R_L}{R_L + R_s} > V_Z = 100 V$$

$$\Rightarrow \text{Breakpoint for } \frac{R_L}{R_L + R_s} = \frac{V_Z}{V_s}$$

$$R_L \left(1 - \frac{V_Z}{V_s}\right) = \frac{V_Z R_s}{V_s}$$

$$R_L = R_s \left(\frac{V_Z}{V_s}\right) \left(\frac{V_s}{V_s - V_Z}\right) = R_s \left(\frac{V_Z}{V_s - V_Z}\right)$$

$$\Rightarrow R_L > 1500 \Omega \left(\frac{100}{50}\right) = \underline{\underline{3 \text{ k}\Omega}}$$


So we get constant V_Z for $R_L > 3 \text{ k}\Omega$

b) For $R_L = 10 \text{ k}\Omega$, solve $\frac{R_L}{R_L + R_s} = \frac{V_Z}{V_s} \Rightarrow V_s = V_Z \frac{(R_L + R_s)}{R_L}$

$$V_s = 100 \left(\frac{1500 + 10^4}{10^4}\right)$$

$$\boxed{V_s > 115 V}$$

(6)

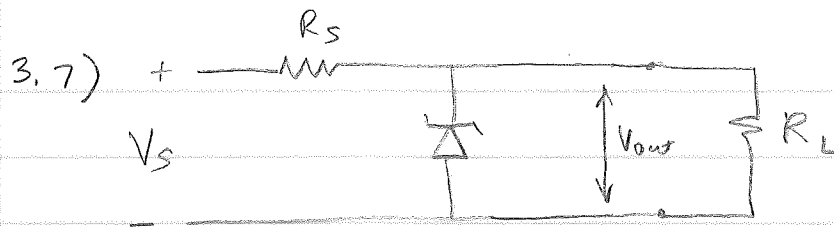

$$V_s = 30\text{ V}$$

$$R_s = 300\ \Omega$$

$$V_z = 15\text{ V}$$

Vary R_L to vary I_L

Want V_{out} vs I_L

Same expressions as in the previous problem apply

$$R_L > R_s \left(\frac{V_z}{V_s - V_z} \right) \text{ gives minimum } R_L \text{ for regulation}$$

$$R_L > 300 \left(\frac{15}{30 - 15} \right) = 300\ \Omega$$

$$\text{At this } R_L, I_L = \frac{15\text{ V}}{R_L} = 50\text{ mA}$$

For larger R_L , I_L is smaller, so for 50 mA or less, voltage is regulated to $V_{out} = V_z$

For $R_L < 300\ \Omega$, I_L is larger and zener not conducting


$$I_L = \frac{V_s}{R_s + R_L} \Rightarrow (R_s + R_L) I_L = V_s$$

$$I_L R_L = V_s - I_L R_s$$

$$V_{out} = I_L R_L$$

$$V_{out} = V_s - I_L R_s$$

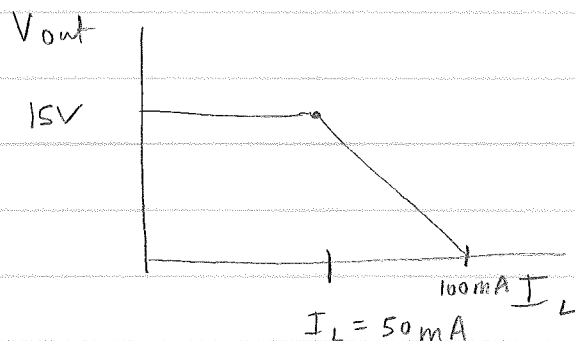so V_{out} vs I_L is straight line with slope $-R_s$.



$$V_{out} = 0 \text{ at}$$

$$I_L = V_s / R_L$$

$$= \frac{30\text{ V}}{300} = 100\text{ mA}$$