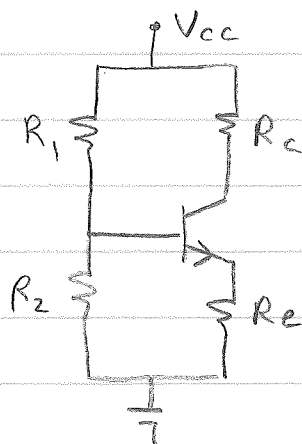


Homework #9 Solutions

4.2) Universal transistor DC bias circuit



$$V_{cc} = 15 \text{ V}$$

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 2.2 \text{ k}\Omega$$

$$R_c = 680 \Omega$$

$$R_e = 100 \Omega$$

$$\beta = 200$$

$$V_{be} = 0.72 \text{ V}$$

Operating point: want I_c, I_b, V_{ce}

$$V_{eq} = \left(\frac{R_2}{R_1 + R_2} \right) V_{cc}$$

$$V_{eq} = \left(\frac{2.2}{12.2} \right) (15 \text{ V}) = \underline{\underline{2.7 \text{ V}}}$$


$$I_b = \frac{V_{eq} - V_{be}}{R_{eq} + (\beta + 1)R_e}, \quad R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 \cdot (2.2)}{12.2} = 1.8 \text{ k}\Omega$$

$$I_b = \frac{2.7 - 0.72}{(1.8 \times 10^3) + (201)(100)} = \underline{\underline{9.04 \times 10^{-5} \text{ A}}}$$



$$I_c = 200 I_b = \underline{\underline{18.1 \text{ mA}}}$$

$$\begin{aligned} V_{ce} &= V_{cc} - I_c \left(R_c + \frac{\beta + 1}{\beta} R_e \right) \\ &= 15 - (18.1 \times 10^{-3}) \left[(680) + \frac{201}{200} (100) \right] \\ V_{ce} &= \underline{\underline{0.873 \text{ V}}} \end{aligned}$$

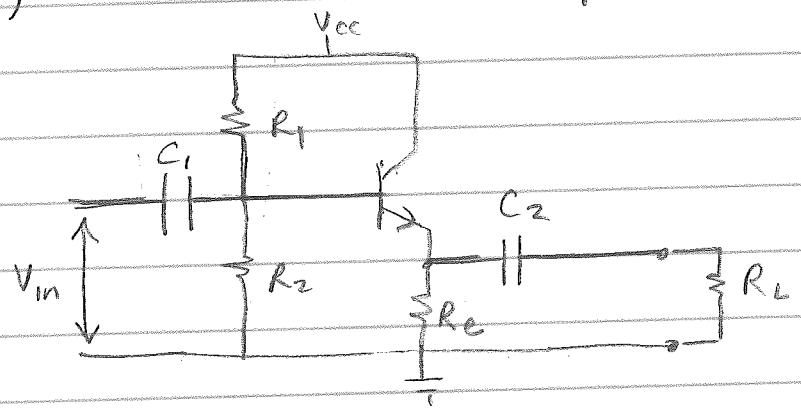4.5) Common-collector amp : want g , Z_{in}



AC equivalent is

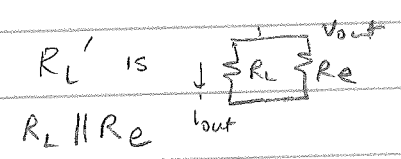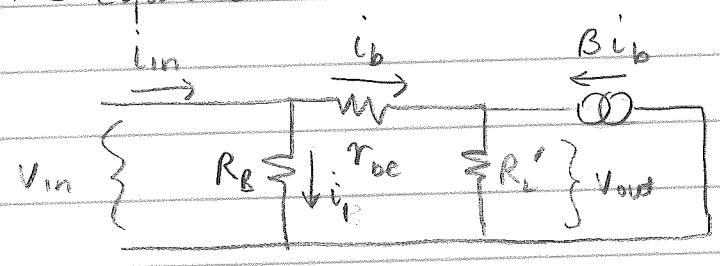

I_{out} is current through R_L

Current gain $g = \frac{I_{out}}{I_{in}}$

$I_{out} = V_{out} / R_L$

1. $g = \frac{V_{out} / R_L}{I_{in}}$ $V_{out} = \underbrace{(i_b + \beta i_b)}_{\text{total current through } R_L' \text{ equiv}} R_L'$

$\Rightarrow g = \frac{(i_b + \beta i_b) R_L' / R_L}{I_{in}}$

$I_{in} = \underbrace{\frac{V_{in}}{R_B}}_{i_i} + i_b$

$V_{in} = \underbrace{i_b r_{be}}_{\text{drop across } r_{be}} + (i_b + \beta i_b) R_L'$

$\Rightarrow I_{in} = \frac{1}{R_B} (i_b r_{be} + (\beta + 1) i_b R_L') + i_b$

$\Rightarrow g = \frac{R_B (1 + \beta) i_b (R_L' / R_L)}{[i_b r_{be} + (\beta + 1) i_b R_L' + i_b R_B]}$

$R_L' = \frac{R_E R_L}{R_E + R_L}$

$R_L' / R_L = R_E / (R_E + R_L)$

$g = (\beta + 1) R_B \left(\frac{R_E}{R_E + R_L} \right) \frac{1}{[r_{be} + R_B + (\beta + 1) R_L']}$

matching eqn 4.35

Input impedance

$$Z_{in} = \frac{V_{in}}{I_{in}}$$


$$Z_{in} = \frac{j\omega r_{be} + (\beta+1)j\omega R_L'}{\frac{1}{R_B}(j\omega r_{be} + (\beta+1)j\omega R_L') + j\omega}$$

$$Z_{in} = \frac{(r_{be} + (\beta+1)R_L') R_B}{(r_{be} + (\beta+1)R_L' + R_B)}$$


matching eqn

4.36

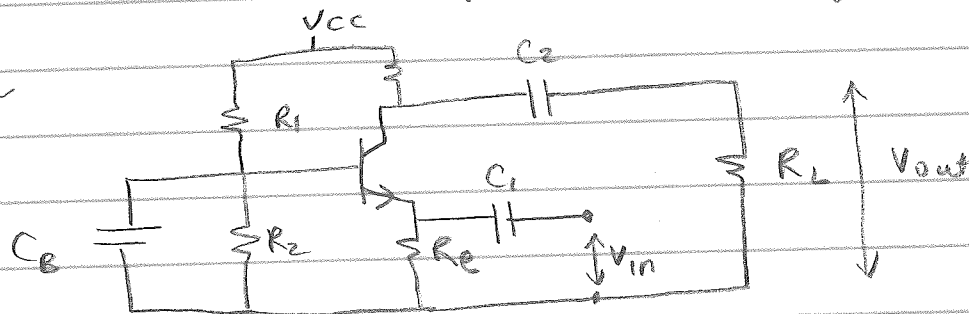4.6) Common-base amplifier : a, g, Z_{in}, Z_{out}



AC equivalent

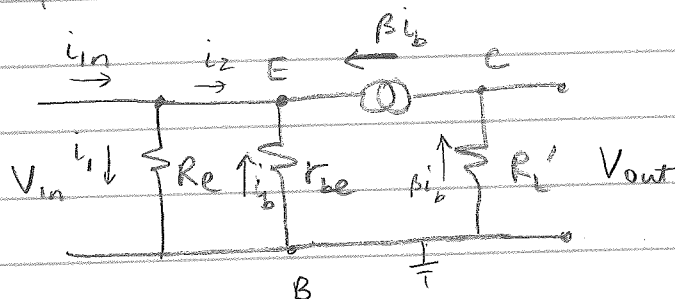

$$R_L' = R_C \parallel R_L$$

$$R_L' = \frac{R_C R_L}{R_C + R_L}$$

Voltage gain

$$a = \frac{V_{out}}{V_{in}} = \frac{-(\beta i_b) R_L'}{-r_{be} i_b}$$

$$V_{out} = -\beta i_b R_L'$$

$$V_{in} = -r_{be} i_b$$

$$\Rightarrow a = \frac{\beta R_L'}{r_{be}} \text{ matches 4.38}$$

i_{out} = current through R_L

Current gain $g = \frac{i_{out}}{i_{in}} = \frac{V_{out}/R_L}{i_1 + i_2}$

$$i_{in} = i_1 + i_2$$

$$i_2 = -(\beta + 1) i_b$$

$$i_1 = \frac{V_{in}}{R_E} = -\frac{r_{be} i_b}{R_E}$$

$$i_{in} = -i_b \left(\frac{r_{be}}{R_E} + (\beta + 1) \right)$$

$$g = \frac{-\beta i_b \frac{R_C R_L}{R_C + R_L}}{-i_b \left(\frac{r_{be}}{R_E} + (\beta + 1) \right)} \Rightarrow g = \beta \left(\frac{R_C R_L}{R_C + R_L} \right) \left(\frac{1}{r_{be} + (\beta + 1) R_E} \right)$$

matches 4.39

Input impedance

$$Z_{in} = \frac{U_{in}}{i_{in}} = \frac{-r_{be} i_b}{-i_b \left(\frac{r_{be}}{R_e} + (\beta + 1) \right)}$$

$$Z_{in} = \frac{r_{be} R_e}{r_{be} + (\beta + 1) R_e}$$

matches 4.40

Output impedance

$$Z_{out} = \frac{U_{out}(\text{open})}{i_{out}(\text{short})} = \frac{-\beta i_b R_c}{-\beta i_b} = R_c$$


$\rightarrow R_c = \infty \Rightarrow R_c' = R_c$
 $\rightarrow (R_c = 0)$
 $\rightarrow -\beta i_b$

$$\Rightarrow Z_{out} = R_c$$

matches 4.41

(6)

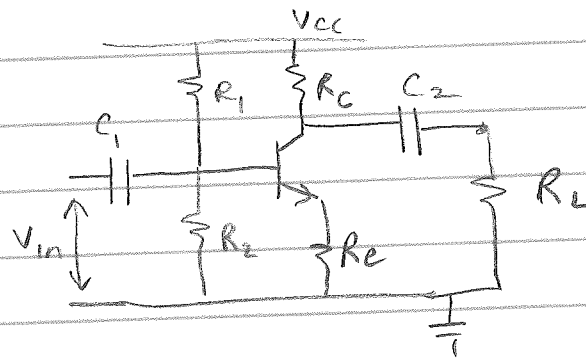4.7) Circuit of Problem 2 configured as CE amp.



DC bias

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 2.2 \text{ k}\Omega$$

$$R_C = 680 \Omega$$

$$R_E = 100 \Omega$$

$$\beta = 200$$

$$V_{BE} = 0.72 \text{ V}$$

$$R_L = 1 \text{ k}\Omega$$

Voltage gain $a = \frac{-\beta R_L'}{r_{be} + (\beta + 1)R_E}$

$$R_L' = R_L \parallel R_C = \frac{(10^3)(680)}{680 + 10^3} = 404.8 \Omega$$

What is r_{be} ? Use eqn 2.6

OK $\rightarrow$ to neglect since $r_{be} < (\beta + 1)R_E$

$$r_{be} = \frac{0.025}{I_B} = \frac{0.025}{9.04 \times 10^{-5}} = 277 \Omega$$


$$a = \frac{-200(404.8)}{277 + (201)(100)} = \underline{\underline{-3.97}}$$

Current gain $g = -\beta \left(\frac{R_B}{R_B + r_{be} + (\beta + 1)R_E} \right) \left(\frac{R_C}{R_C + R_L} \right)$

$$R_B = R_1 \parallel R_2 = \frac{(10)(2.2)}{12.2} = 1.8 \text{ k}\Omega$$

$$g = -200 \left(\frac{1.8 \times 10^3}{1.8 \times 10^3 + 277 + (201)(100)} \right) \left(\frac{680}{680 + 1000} \right) = \underline{\underline{-6.57}}$$

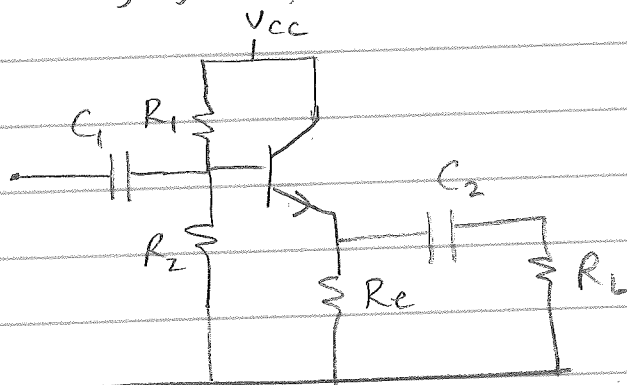4.8) Transistor amp w/ $\alpha \sim 1$, $g \sim 100$
 For unity gain, use emitter follower (CC amp)



We need to find the operating point
 for the transistor with specs in Fig 4.3.1
 which has $\beta \sim 100$ in plateau regime

We will get
$$g = (\beta + 1) \left(\frac{R_B}{R_B + r_{be} + (\beta + 1)R_L'} \right) \left(\frac{R_e}{R_e + R_L} \right)$$

For small load and largish R_B

we will get

$$g \sim (\beta + 1) \frac{R_B}{R_B} \frac{R_e}{R_e} \sim \beta$$

So just need to choose R_1, R_2, R_e for

$I_b \sim$ few 10's of μA to be

in the linear operating regime

Take $\left[\begin{array}{l} I_b = 20 \mu A \\ I_c = 3.6 \text{ mA} \\ V_{ce} = 4 \text{ V} \end{array} \right] \rightarrow \text{from Fig 4.3.1 (other points OK)}$

Assume $V_{be} = 0.6 \text{ V}$ (V_{pn})

Pick $V_{cc} = 15 \text{ V}$

Pick $R_1 = 10 \text{ k}\Omega, R_2 = 100 \text{ k}\Omega$

$$R_{eq} = \frac{(10)(100)}{110} = 9 \text{ k}\Omega, V_{eq} = \frac{100 \cdot V_{cc}}{110} = 13.6 \text{ V}$$

This is the goal,
 select components
 for this

$$V. \quad I_b = \frac{V_{eq} - V_{be}}{R_{eq} + (\beta + 1)R_e}$$

Solve for R_e to get desired $I_b = 20 \mu A$

$$R_{eq} + (\beta + 1)R_e = \frac{V_{eq} - V_{be}}{I_b}$$

$$R_e = \left(\frac{V_{eq} - V_{be}}{I_b} - R_{eq} \right) \frac{1}{(\beta + 1)}$$

$$R_e = \left(\frac{13.6V - 0.6V}{20 \times 10^{-6}} - 9.1 \times 10^3 \right) = \underline{\underline{3.3 k\Omega}}$$

check: $V_{ce} = V_{cc} - I_c \left(\frac{\beta + 1}{\beta} R_e \right) = 3V,$

still OK for
being in the
operating regime

So we have chosen

$$\begin{cases} R_1 = 10 k\Omega \\ R_2 = 100 k\Omega \\ R_e = 3.3 k\Omega \end{cases}$$

Assume R_e small

(Other choices OK)